


The final exam of " Introduction to Electronics" on 29.05.2020

In the final exam we have **only 6** questions similar to the following:


Student's name:

Student's ID No:

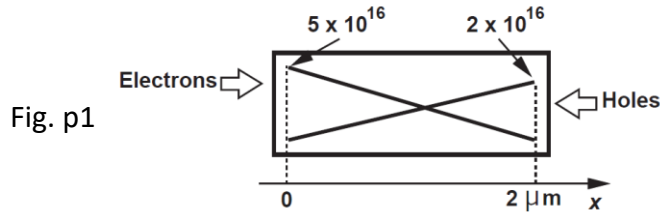
- Fig. p1 shows a p-type bar of silicon that is subjected to electron injection from the left and hole injection from the right. Determine the total current flowing through the device if the cross-section area is equal to $1 \mu\text{m} \times 1 \mu\text{m}$.



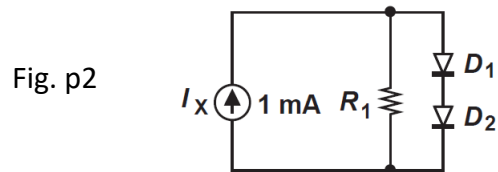
- In the circuit of Fig. p2, determine the value of R_1 such that this resistor carries 0.5 mA. Assume $I_S = 5 \times 10^{-16} \text{ A}$ for each diode.



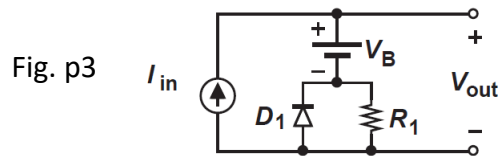
- Plot V_{out} as a function of I_{in} for the circuits shown in Fig. p3. Assume a constant voltage diode model.




- A full-wave rectifier is driven by a sinusoidal input $V_{\text{in}} = V_0 \cos \omega t$, where $V_0 = 3 \text{ V}$ and $\omega = 2\pi(60 \text{ Hz})$. Assuming $V_{D,\text{on}} = 800 \text{ mV}$, determine the ripple amplitude with a $1000\text{-}\mu\text{F}$ smoothing capacitor and a load resistance of 30Ω .
- Consider the circuit shown in Fig. p5.
 - If $I_{S1} = 2I_{S2} = 5 \times 10^{-16} \text{ A}$, determine V_B such that $I_X = 1.2 \text{ mA}$.
 - What value of R_C places the transistors at the edge of the active mode?

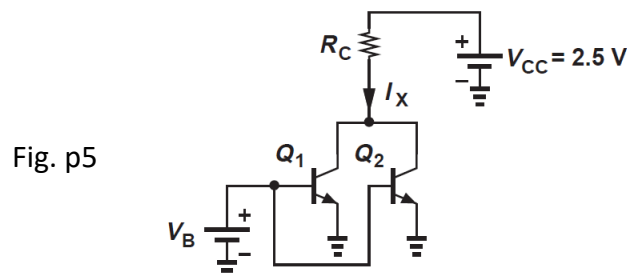

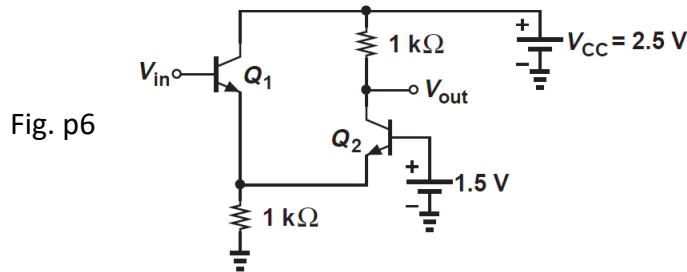
6. Plot the input/output characteristic of the stage shown in Fig. p6 for $0 < V_{in} < 2.5$ V. At what value of V_{in} do Q_1 and Q_2 carry equal collector currents?



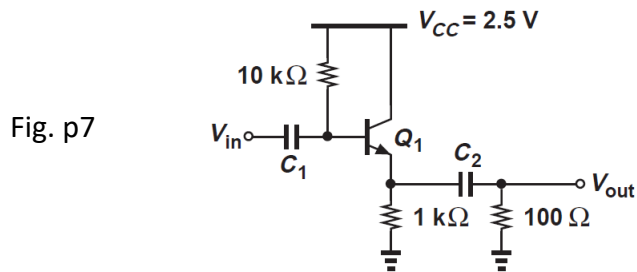
7. Determine the voltage gain of the follower depicted in Fig. p7. Assume $I_S = 7 \times 10^{-16}$ A, $\beta = 100$, and $V_A = 5$ V. (But for bias calculations, assume $V_A = \infty$.) Also, assume the capacitors are very large.



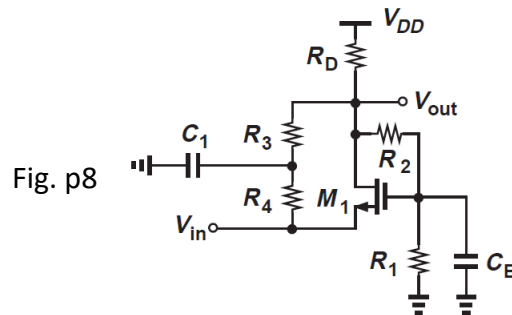8. Calculate the voltage gain of the stage depicted in Fig. p8. Assume $\lambda = 0$ and the capacitors are very large.



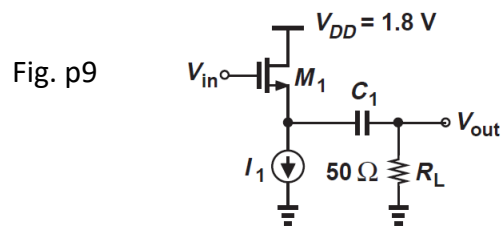9. We wish to design the source follower of Fig. p9 for a voltage gain of 0.8 with a power budget of 3 mW. Compute the required value of W/L . Assume C_1 is very large and $\lambda = 0$.



Wish you full success!

$$\epsilon_{Si}=\epsilon_r \text{ (Si)} \times \epsilon_0=11.7\times 8.85\times 10^{-12} \text{ F/m}, k= 1.38\times 10^{-23} \text{ J/K}, \quad D_n = 34 \text{ cm}^2/\text{s}, D_p = 12 \text{ cm}^2/\text{s},$$

$$I_{tot}=I_s(\exp\frac{V_F}{V_T}-1) \qquad I_s=Aqn_i^2(\frac{D_n}{N_AL_n}+\frac{D_p}{N_DL_p})$$

$$V_0=\frac{kT}{q}\ln\frac{N_A N_D}{n_i^2}.$$

$$C_j=\frac{C_{j0}}{\sqrt{1-\frac{V_R}{V_0}}}, \quad C_{j0}=\sqrt{\frac{\epsilon_{si}q}{2}\frac{N_A N_D}{N_A+N_D}\frac{1}{V_0}}, \qquad \frac{D}{\mu}=\frac{kT}{q}.$$

$$J_{tot}=q(\mu_n n+\mu_p p)E \qquad J_{tot}=q(D_n dn/dx-D_p dp/dx)$$

$$V_R \approx \frac{V_p-V_{D,on}}{R_L} \cdot \frac{T_{in}}{C_1} \approx \frac{V_p-V_{D,on}}{R_L C_1 f_{in}},$$

$$I_p \approx C_1 \omega_{in} V_p \sqrt{\frac{2V_R}{V_p}} + \frac{V_p}{R_L} \approx \frac{V_p}{R_L} (R_L C_1 \omega_{in} \sqrt{\frac{2V_R}{V_p}} + 1)$$

$$I_C=\frac{A_E q D_n n_i^2}{N_E W_B} \left(\exp \frac{V_{BE}}{V_T}-1\right)$$

$$I_C=I_S\exp\frac{V_{BE}}{V_T}$$

$$I_S=\frac{A_E q D_n n_i^2}{N_E W_B} \qquad r_O=\frac{V_A}{I_C}$$

$$V_{TH}=V_{TH0}+\rho\big(\sqrt{2\phi_F+V_{SB}}-\sqrt{2\phi_F}\big)$$

$$I_D=\frac{1}{2}\mu_nC_{ox}\frac{W}{L}\left[2(V_{GS}-V_{TH})V_{DS}-V_{DS}^2\right]$$

$$I_D=\frac{1}{2}\mu_nC_{ox}\frac{W}{L}(V_{GS}-V_{TH})^2(1+\lambda V_{DS}), \qquad r_O=\frac{1}{\lambda I_D}$$

$$R_{on}=\frac{1}{\mu_nC_{ox}\frac{W}{L}(V_{GS}-V_{TH})}.$$

$$g_m=\mu_nC_{ox}\frac{W}{L}(V_{GS}-V_{TH}) \qquad g_m=\frac{2I_D}{V_{GS}-V_{TH}} \qquad g_m=\sqrt{2\mu_nC_{ox}\frac{W}{L}I_D}$$