

# 1 Introduction - Prelab

## 1.1 Biasing of Bipolar Junction Transistor

### 1. Calculations

$$V_{R1} + V_B = 20V$$


$$I_C = 150 I_B$$

$$I_E = I_C + I_B$$

$$V_B = 20 \cdot \frac{R_2}{R_2 + R_1} = 6,23V$$

$$V_E = V_B - V_{BE} = 5,55V$$

$$I_E = \frac{V_E}{R_E} = 11,8\mu A$$

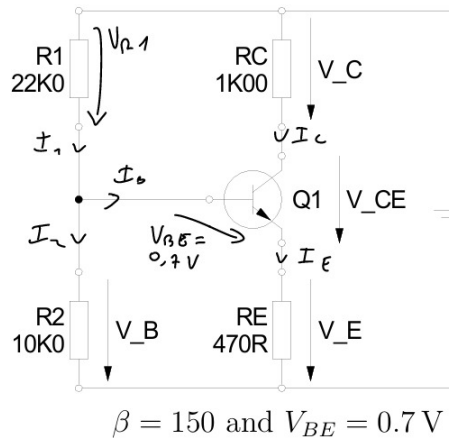

$$\begin{cases} I_C < 150 I_B \\ I_C + I_B = 11,8\mu A \end{cases}$$

$$151 I_B = 11,8\mu A \Rightarrow I_B = 78,1\mu A$$


$$I_C = 150 I_B \rightarrow 11,72\mu A$$

$$V_C = I_C R_C = 11,72V$$

$$V_{CE} = V_{CC} - V_C - V_E = 2,73V$$


- Calculate  $V_B$ ,  $V_E$ ,  $V_{CE}$ , and  $V_C$ .
- Calculate  $I_B$ ,  $I_E$ , and  $I_C$ .

### LTSpice simulation

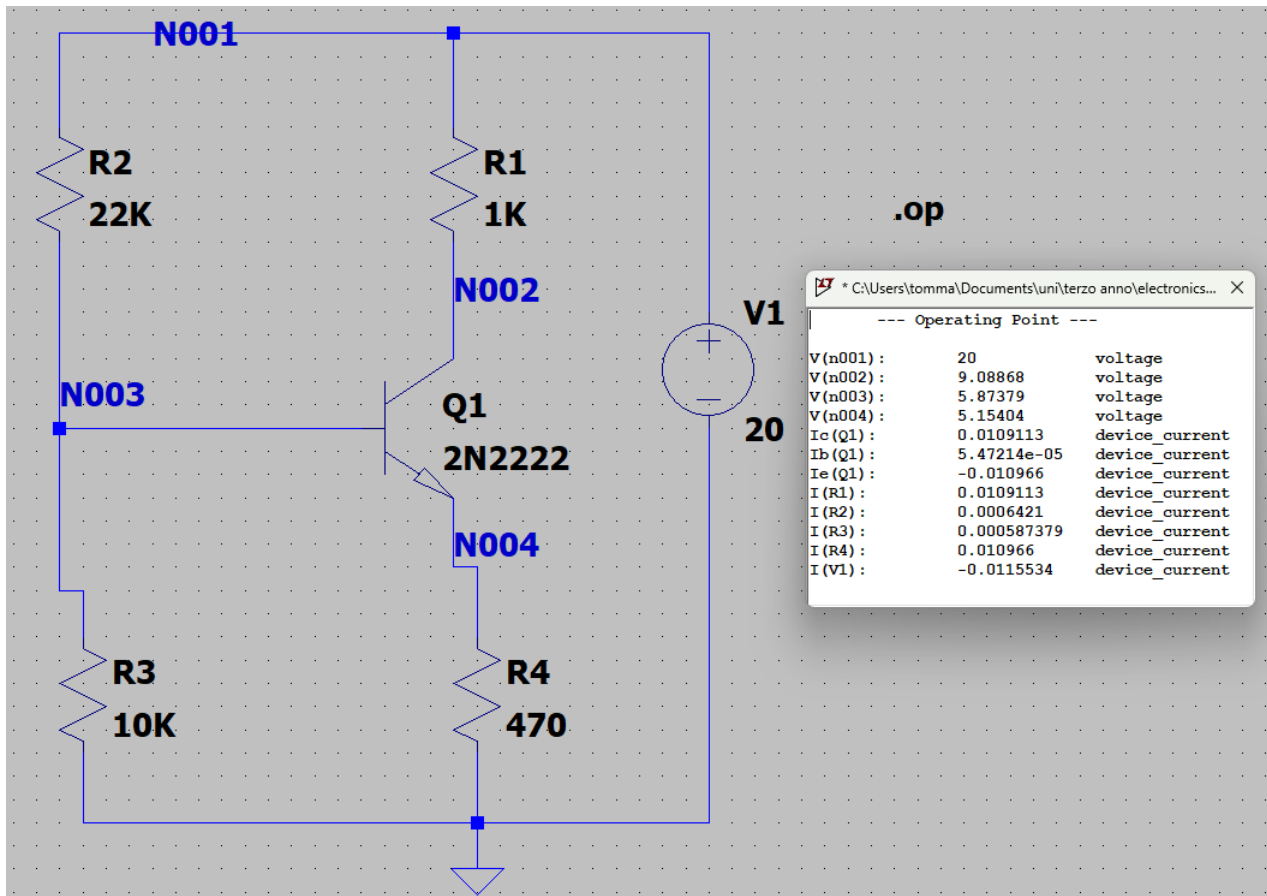


## 1.2 Constant Current Source
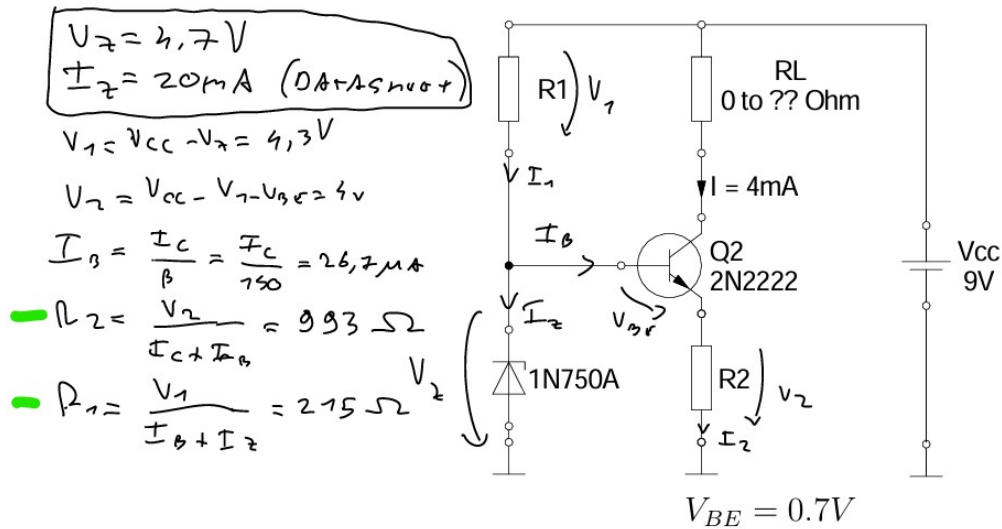
### 1. Calculations and simulation on LTSpice




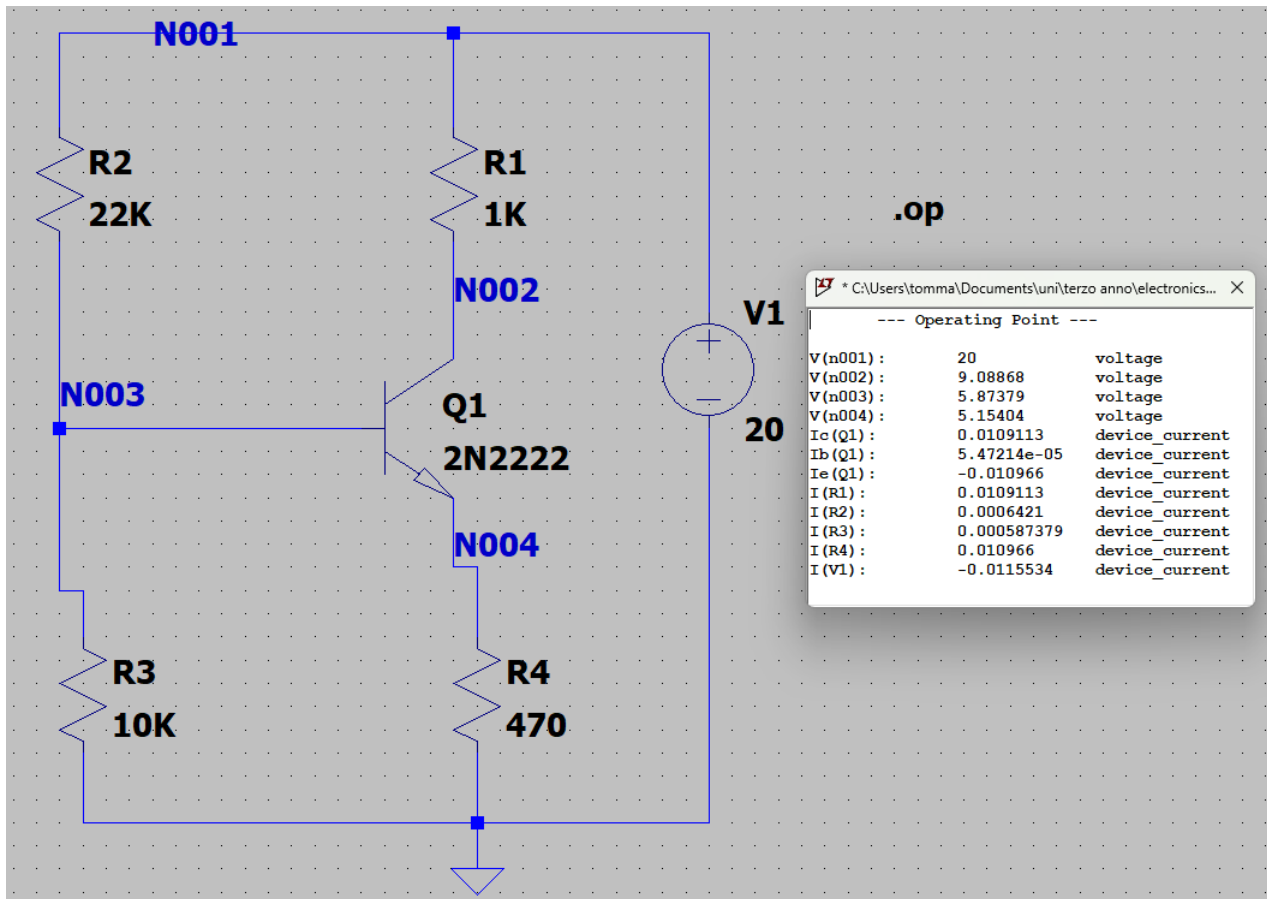2.  $R_1 = 215\Omega$ ,  $R_2 = 993\Omega$




3. To have a constant current  $V_{CE}$  has to be higher than  $0.3V$  (from 2N2222 datasheet) to stay in active mode. So the condition for  $R_L$  is  $V_{RL} < V_{CC} - 0.3V - V_2 = V_{RL} < 4.7V$  so  $R_L$  must be lower than  $\frac{4.7}{0.004} = 1175\Omega$ .

#### 4. Max $R_L$ in LTSpice

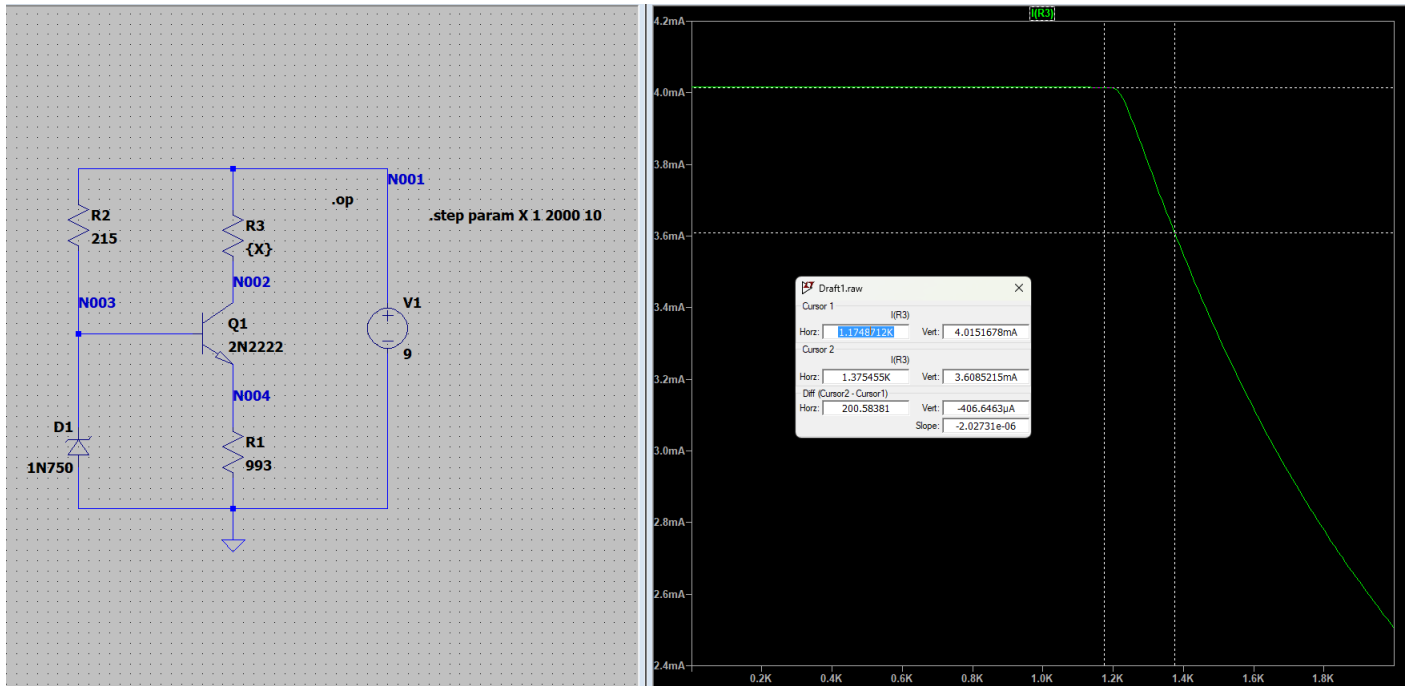

At  $1275\Omega$  the current is 4mA, at  $1375\Omega$  the current is 10% less (3.6mA).

### 1.3 Amplifier circuit

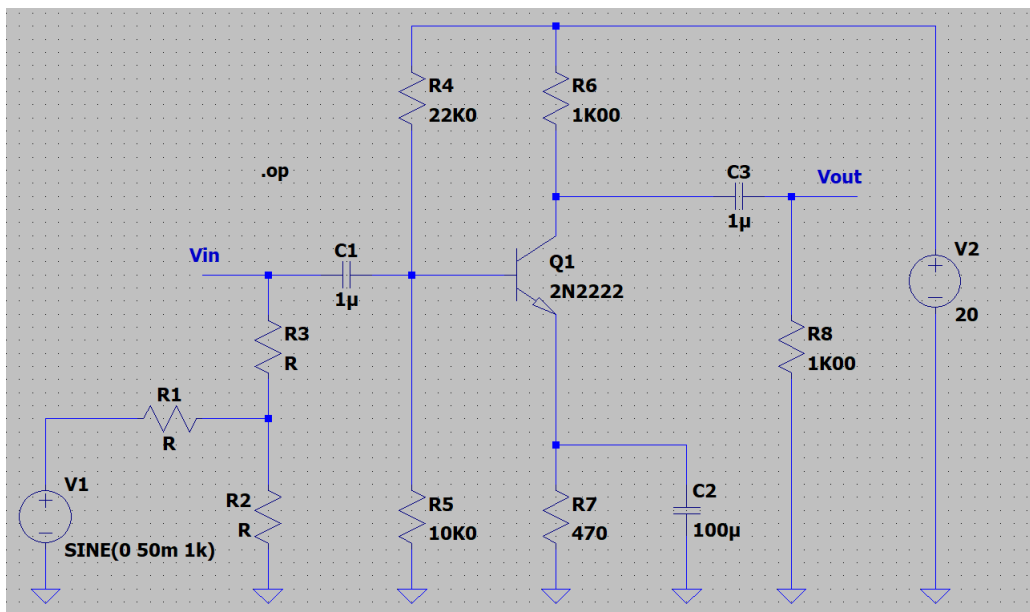


1.

#### 2. DC operation point values


$$I_C = 0.011 \text{ A}, I_B = 54.7 \text{ uA}$$

$$V_B = 5.87\text{V}, V_E = 5.15 \text{ V}, V_C = 9.09\text{V}, V_{BE} = 0.12, V_{CE} = 3.94\text{V}$$

### 3. Transient analysis at 50mV

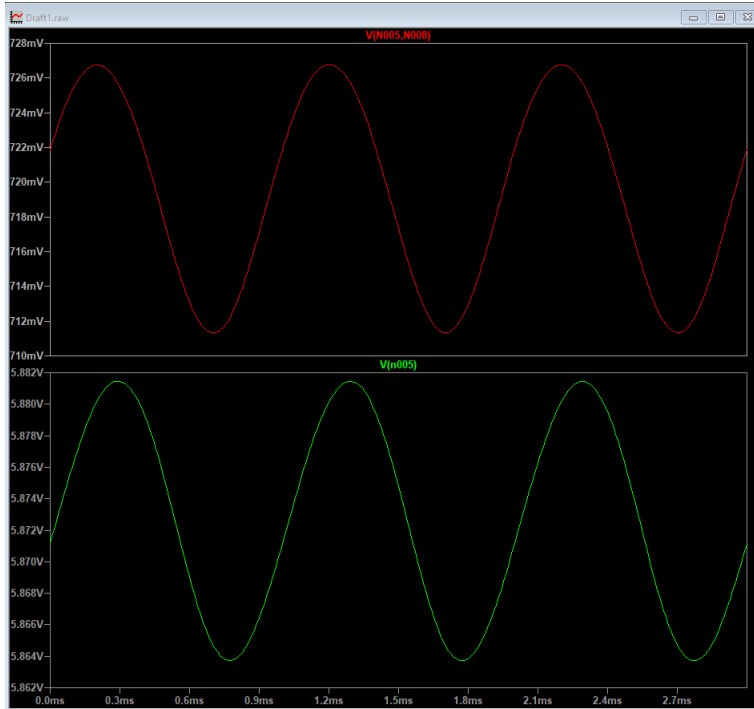

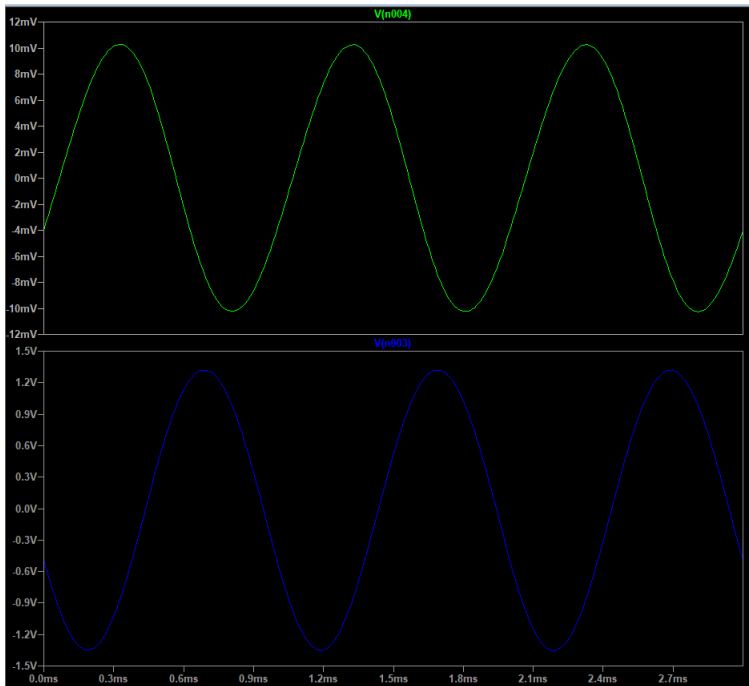
Green line:  $V_B$ : 17.7mV peak to peak, red line:  $V_{BE}$ : 15.4mV peak to peak.



Green line:  $V_i$ : 20.5mV peak to peak, blue line:  $V_o$ : 2.67V.

Gain:  $\frac{V_o}{V_i} = 130$ .

#### 4. Harmonic distortion analysis

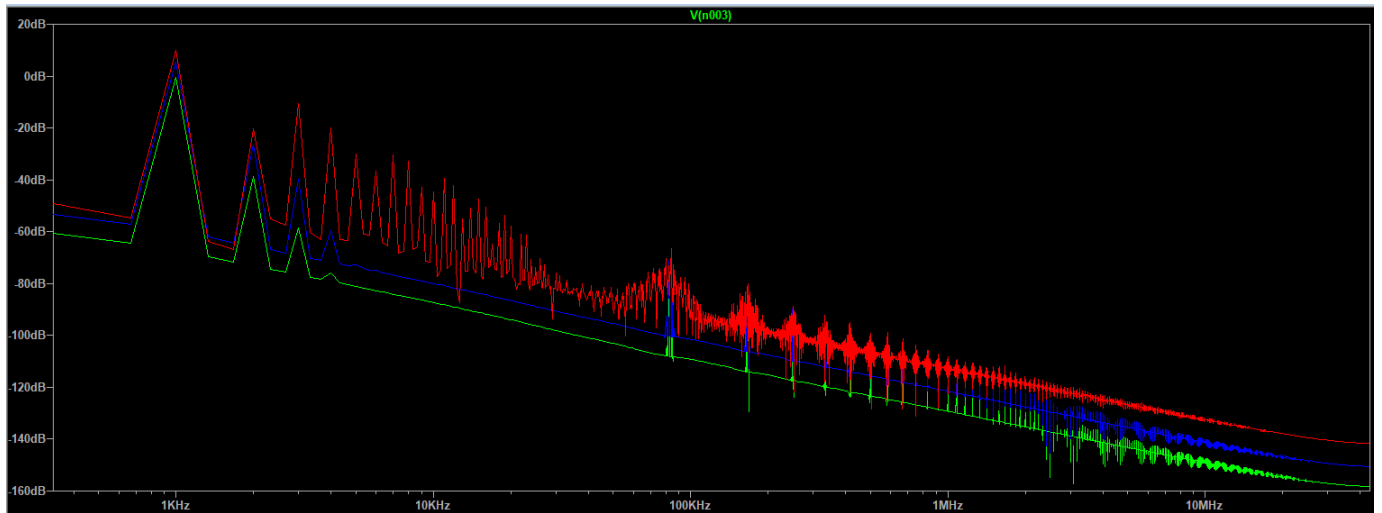

According to the FFT the harmonic distortion is similar between 50mV and 100mV as input amplitude and is much worse when using 200mV.

5. AC analysis

