

# Properties of the Differential Amplifier

Tommaso Bertelli

CO-526-B - Electronics Lab


Instructor Uwe Pagel

24/11/2024

# 1 Introduction - Prelab


## 1.1 Simulation of a Differential Amplifier

1.

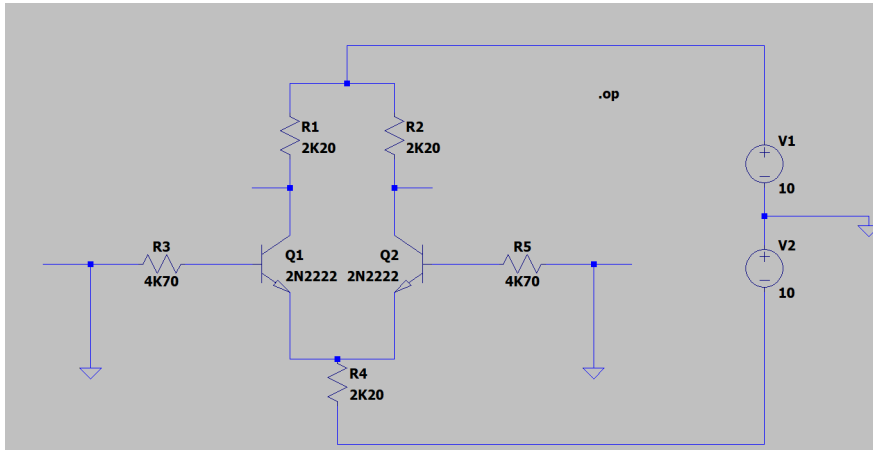



Measured voltages and currents:

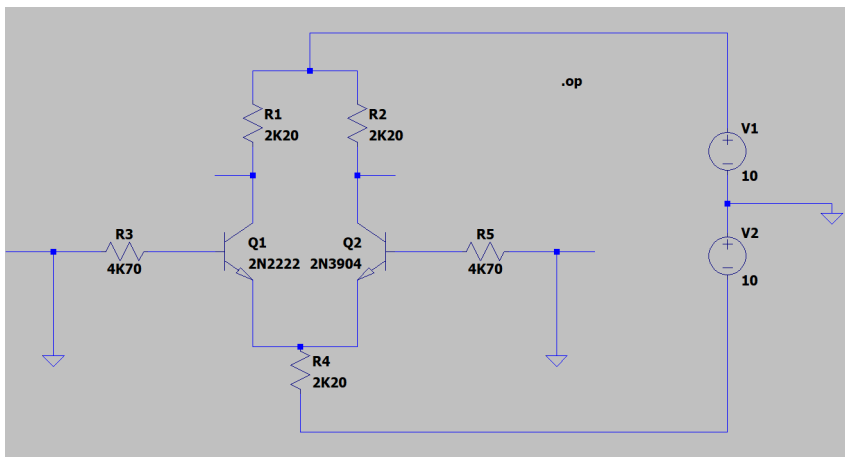$V_{BE} = -47.09 - (-720.71) = 767.8\text{mV}$ ,  $V_C = 5.382\text{V}$ ,  $I_C = 2.099\text{mA}$ ,  $I_E = 2.109\text{mA}$ ,  $I_{RE} = 4.219\text{mA}$ .




By changing one transistor the  $V_{BE}$ ,  $V_C$ ,  $I_C$ ,  $I_E$  values are not symmetric anymore (ex.:  $V_C(\text{Q1}) = 5.911\text{V}$ ,  $V_C(\text{Q2}) = 4.837\text{V}$ ), therefore the circuit cannot work properly.

## 2. Single ended input analysis

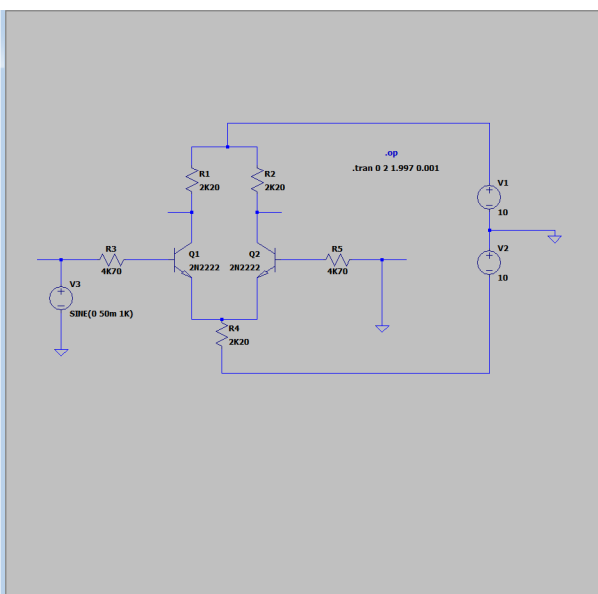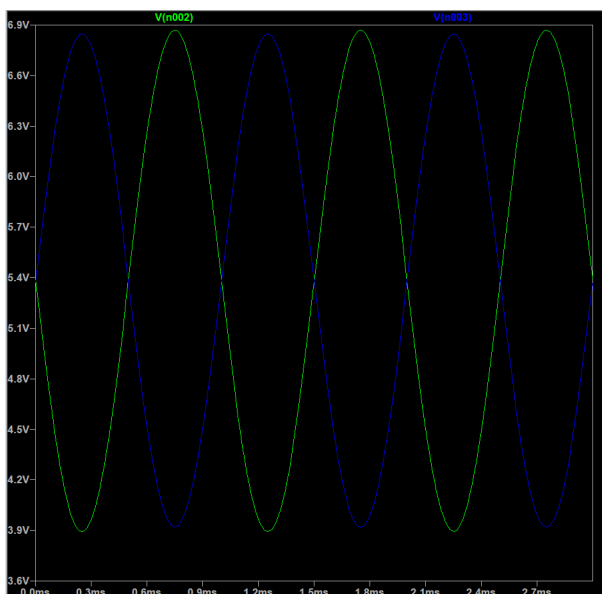

Green line:  $V_C(\text{Q1})$ , blue line:  $V_C(\text{Q2})$ . (peak to peak: 2.923V)

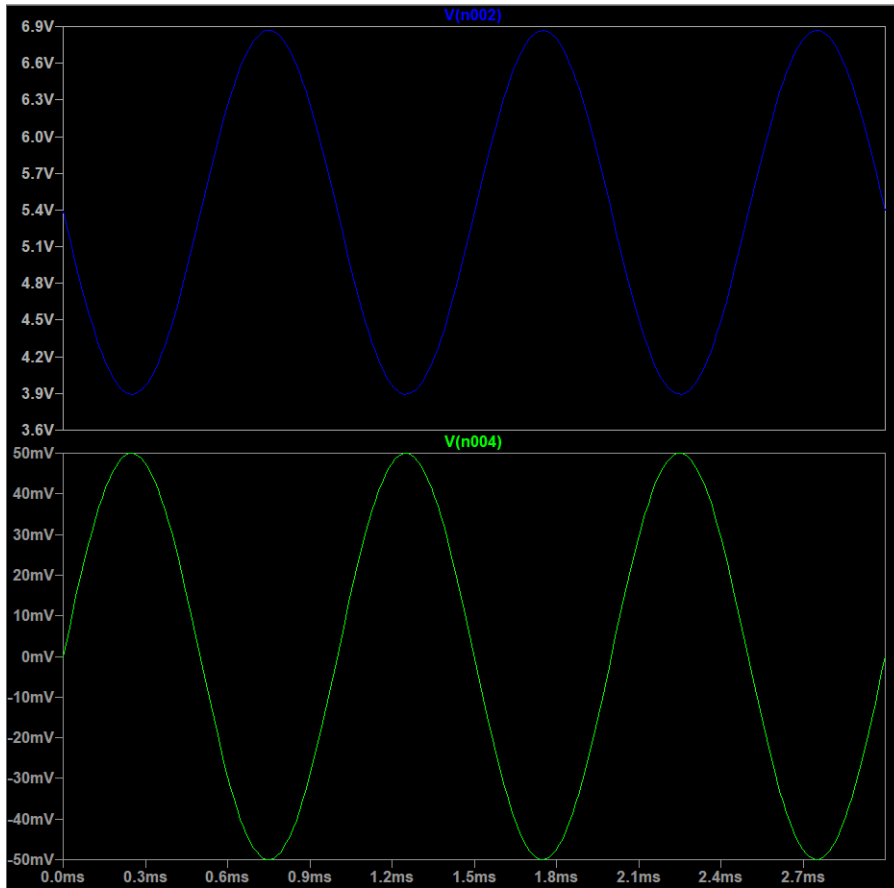To calculate  $A_{V_{diff}}$  I need  $V_{od}$  and  $V_{id}$ .




Top pane:  $V_{o1}$ , bottom pane:  $V_{i1}$

$V_{id} = V_{i1} - V_{i2} = 100\text{mV}$  peak to peak


$V_{od} = V_{o1} = 3\text{V}$  peak to peak

$A_{V_{diff}} = 20\log(\frac{V_{od}}{V_{id}}) = 29.5 \text{ dB}$ .

### 3. Common mode input analysis

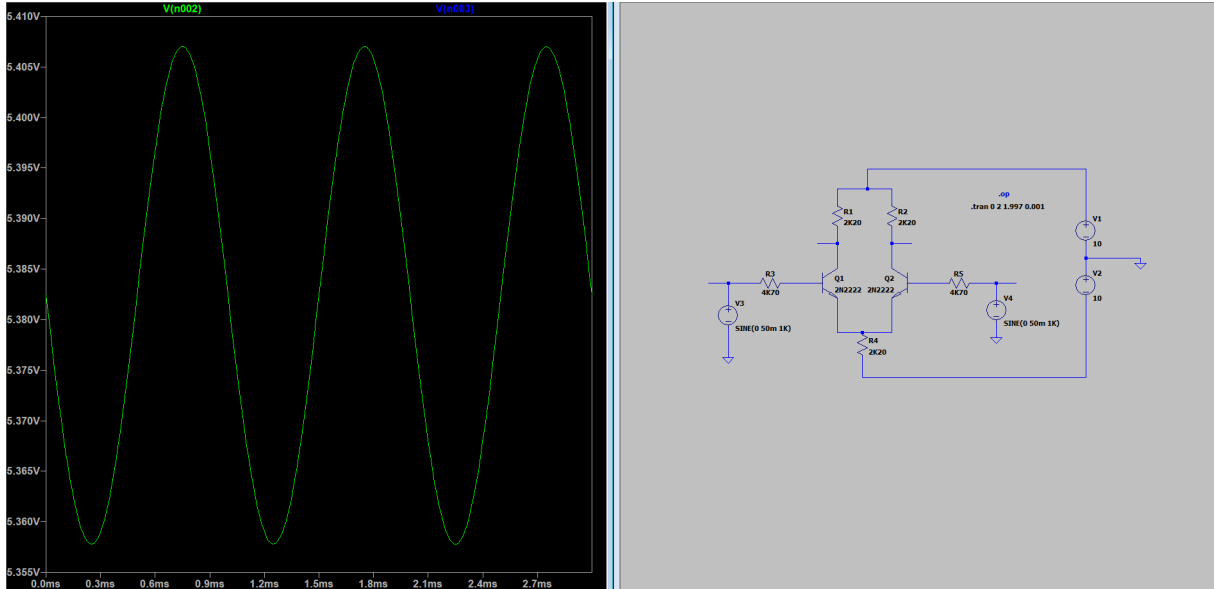

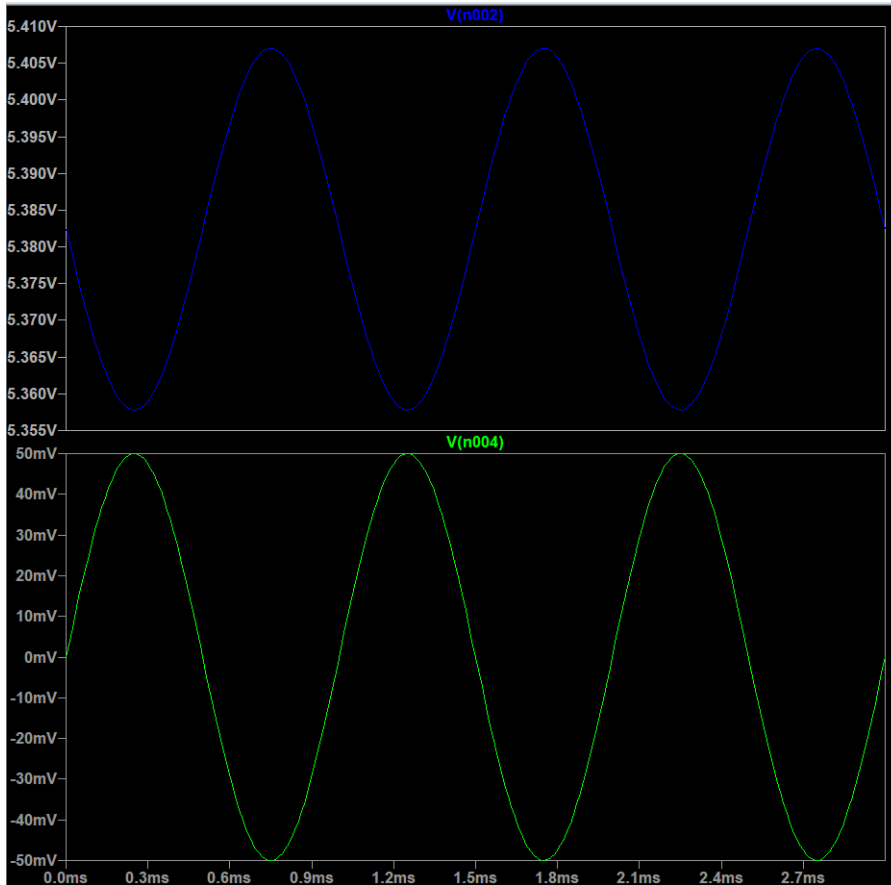$V_C(Q1)$  and  $V_C(Q2)$  are overlapping. (peak to peak: 49.17mV).  
To calculate  $A_{V_{cm}}$  I need  $V_{oc}$  and  $V_{ic}$ .



Top pane:  $V_{o1}$ , bottom pane:  $V_{i1}$

$$V_{ic} = (V_{i1} + V_{i2})/2 = 100\text{mV peak to peak}$$

$$V_{oc} = V_{o1} = 49.18\text{mV peak to peak}$$


$$A_{V_{cm}} = 20\log\left(\frac{V_{oc}}{V_{ic}}\right) = -6.16 \text{ dB.}$$

### 4. Common mode rejection

$$CMRR = 20\log\left(\frac{A_{V_{diff}}}{A_{V_{cm}}}\right) = 35.7\text{dB.}$$

current source: 4.219 from top to bottom

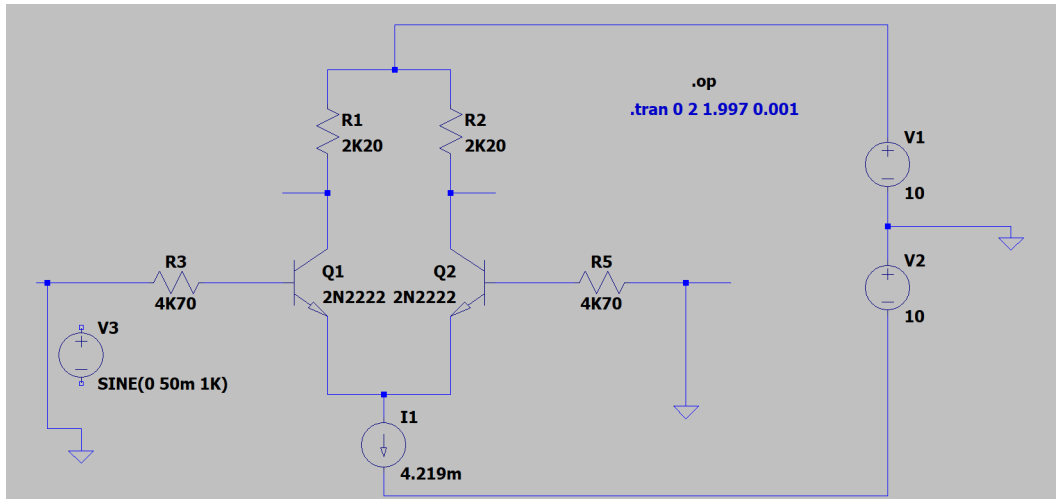
## 5. Replacing R4 by equivalent current source



## 6. Analyses using the current source

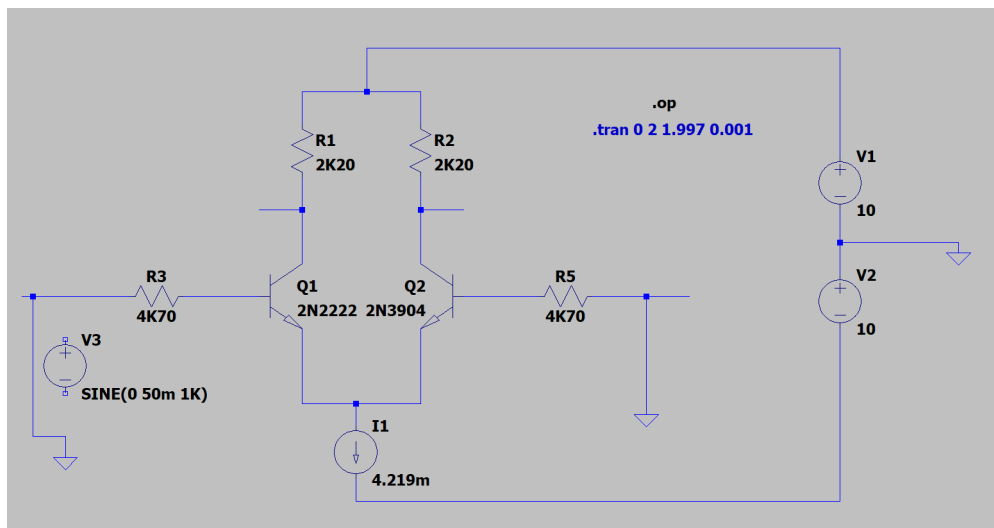
### (a) DC operation point analysis

$V_{BE} = -47.11 - (-720.74) = 767.85\text{mV}$ ,  $V_C = 5.381\text{V}$ ,  $I_C = 2.099\text{mA}$ ,  $I_E = 2.109\text{mA}$ ,  $I_{RE} = 4.219\text{mA}$ . (current source)




By changing one transistor the  $V_{BE}$ ,  $V_C$ ,  $I_C$ ,  $I_E$  values are not symmetric anymore (ex.:  $V_C(Q1) = 5.913\text{V}$ ,  $V_C(Q2) = 4.841\text{V}$ ), therefore the circuit cannot work properly.

(b) Single ended input analysis

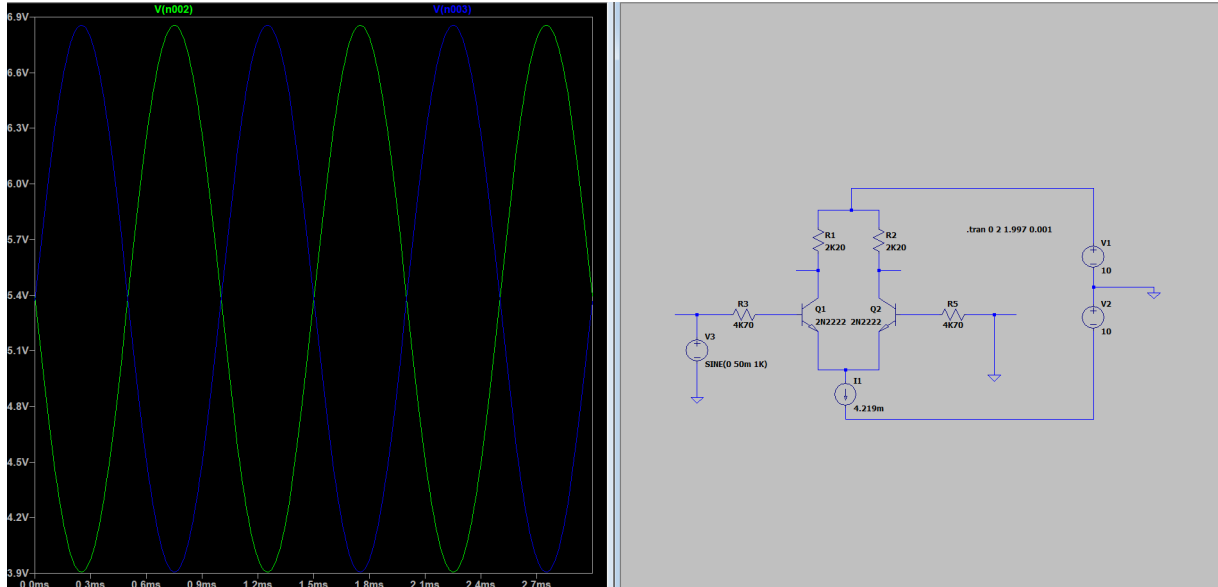

Green line:  $V_C(Q1)$ , blue line:  $V_C(Q2)$ . (peak to peak: 2.95V)

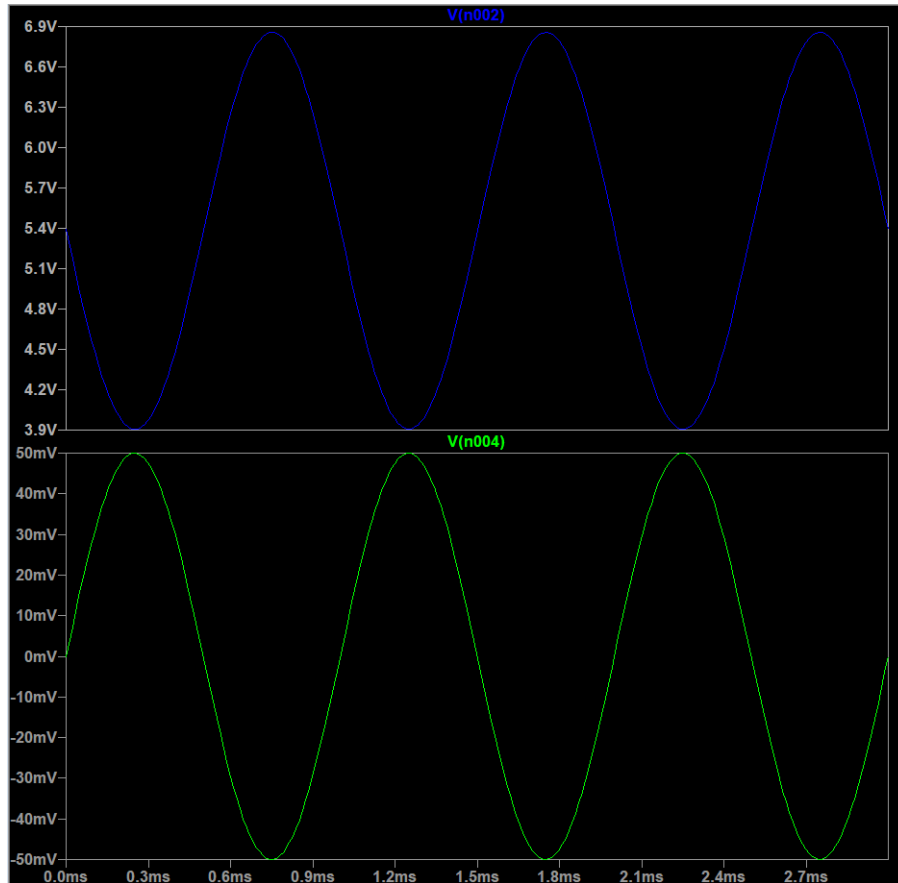To calculate  $A_{V_{diff}}$  I need  $V_{od}$  and  $V_{id}$ .




Top pane:  $V_{o1}$ , bottom pane:  $V_{id}$

$$V_{id} = V_{i1} - V_{i2} = 100\text{mV peak to peak}$$

$$V_{od} = V_{o1} = 2.95\text{V peak to peak}$$


$$A_{V_{diff}} = 20\log\left(\frac{V_{od}}{V_{id}}\right) = 29.4 \text{ dB}.$$

(c) Common mode input analysis

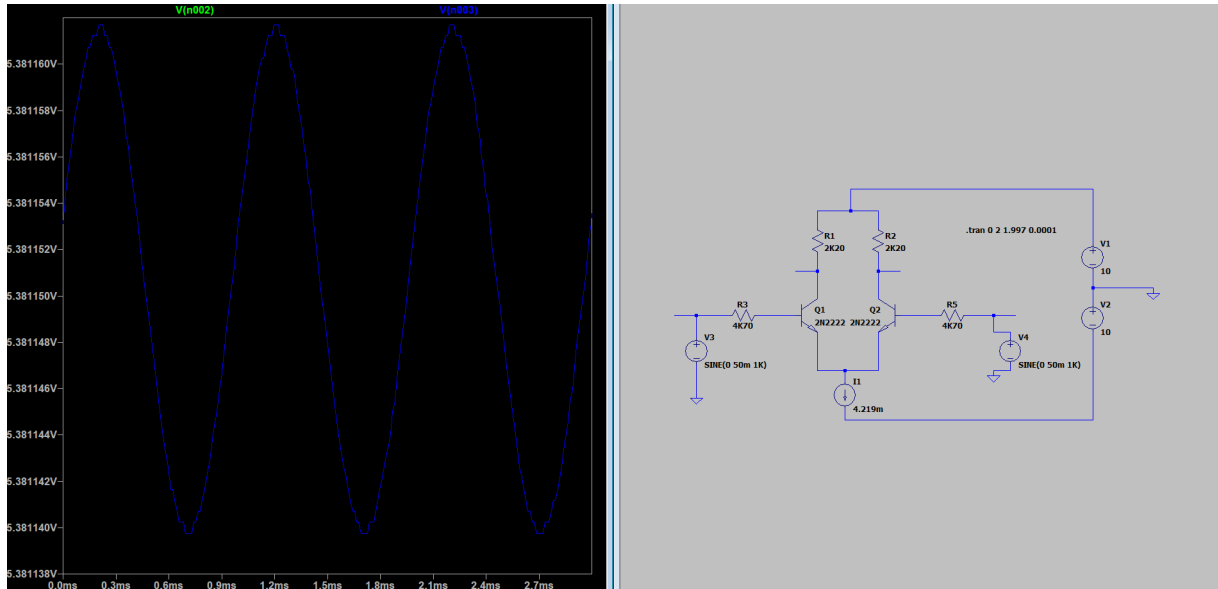

$V_C(Q1)$  and  $V_C(Q2)$  are overlapping. (peak to peak:  $21.93\mu\text{V}$ ).

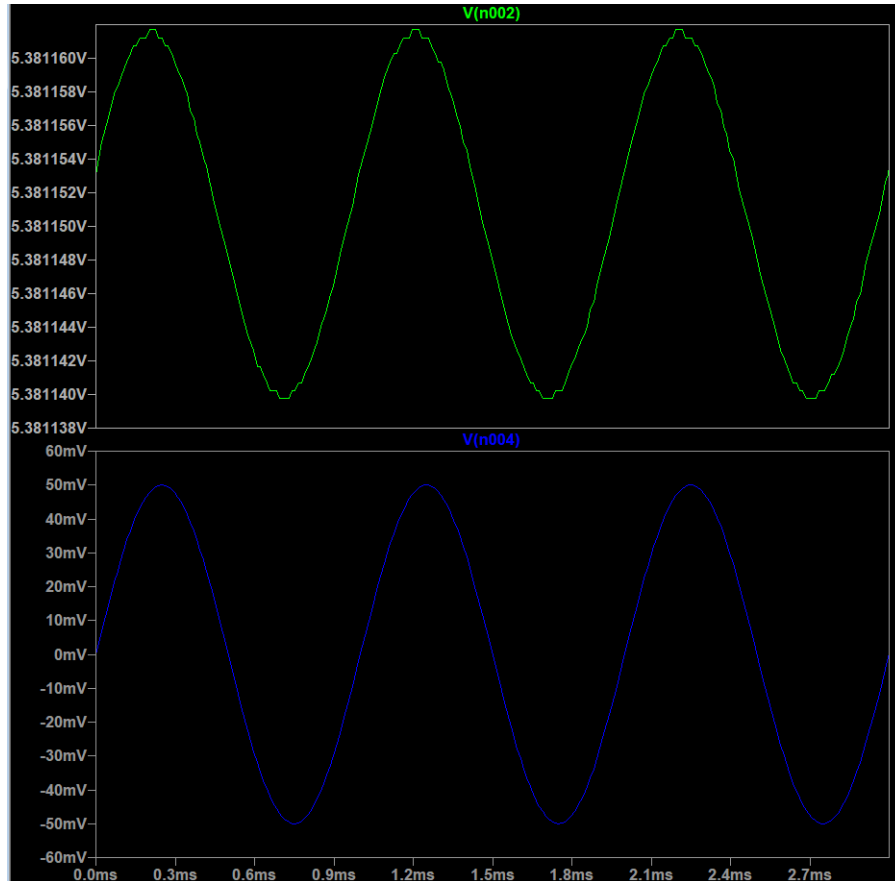To calculate  $A_{V_{cm}}$  I need  $V_{oc}$  and  $V_{ic}$ .



Top pane:  $V_{o1}$ , bottom pane:  $V_{i1}$

$$V_{ic} = (V_{i1} + V_{i2})/2 = 100\text{mV peak to peak}$$

$$V_{oc} = V_{o1} = 21.93\mu\text{V peak to peak}$$

$$A_{V_{cm}} = 20\log\left(\frac{V_{oc}}{V_{ic}}\right) = -73.28 \text{ dB.}$$

(d) Common mode rejection


$$CMRR = 20\log\left(\frac{A_{V_{diff}}}{A_{V_{cm}}}\right) = 102.6\text{dB.}$$

## 2 Experimental Set-up and Results


### 2.1 Differential amplifier using a fixed emitter resistor

1. COMPARE DC VALUES
2. CMRR calculation

Output voltage in single ended mode:

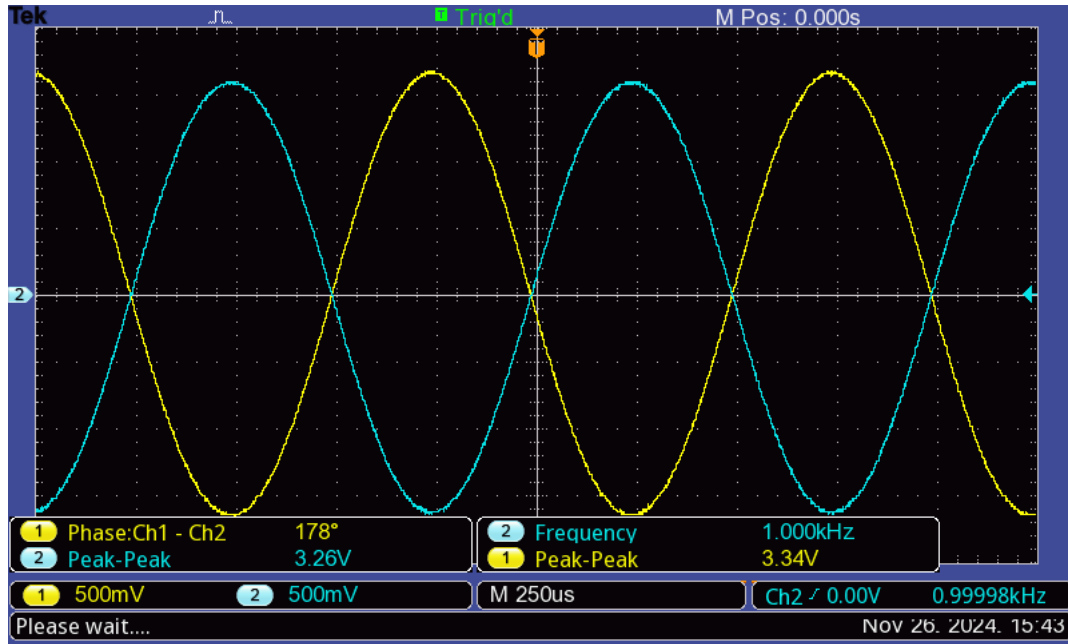

Output voltage in common mode:

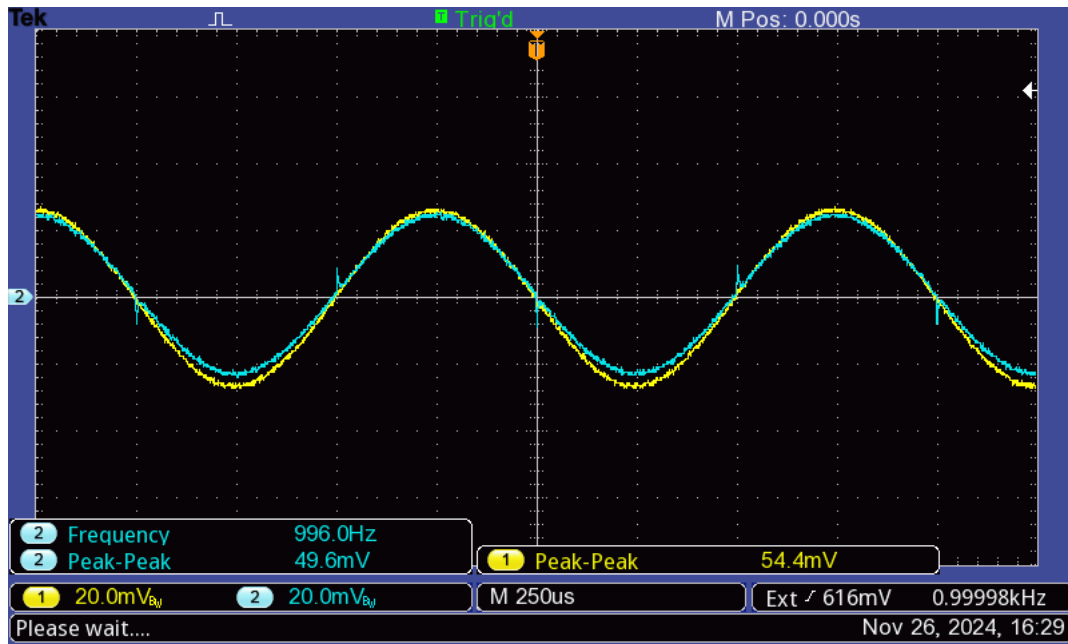

Since the input is 100mV peak to peak

$$V_{vdm} = 20 \log \frac{3300}{100} = 30.4 \text{dB}$$

$$V_{vcm} = 20 \log \frac{51.5}{100} = -5.76 \text{dB}$$


$$\text{CMRR} = 20 \log \frac{V_{vdm}}{V_{vcm}} = \frac{3300}{\frac{51.5}{100}} = 36.1 \text{dB}$$




## 2.2 Differential amplifier using a current source

1. COMPARE DC VALUES
2. CMRR calculation

Output voltage in single ended mode:

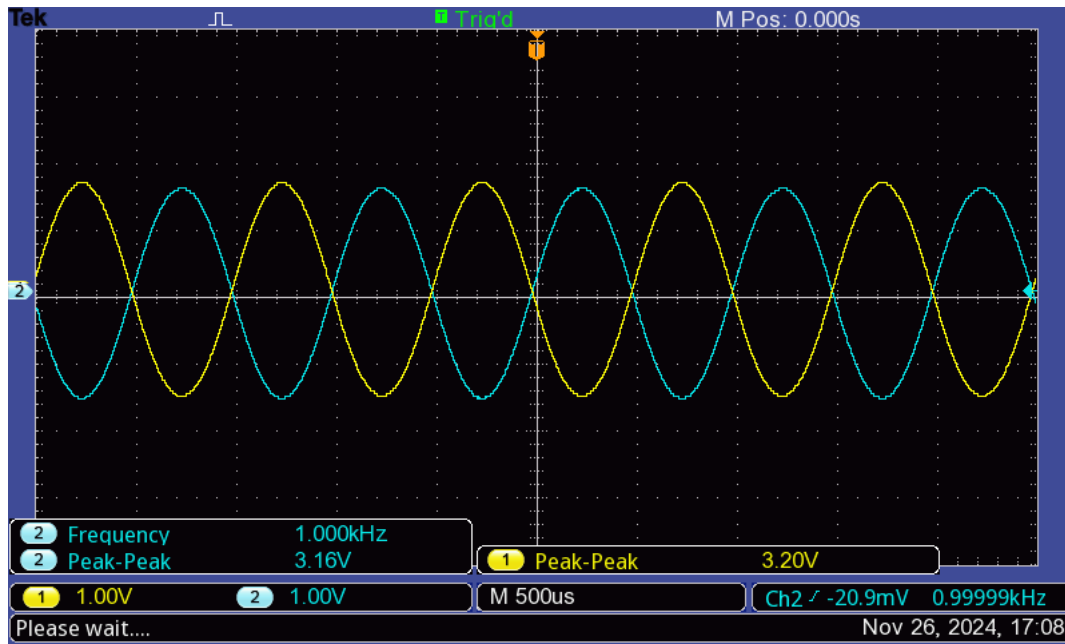

Output voltage in common mode:

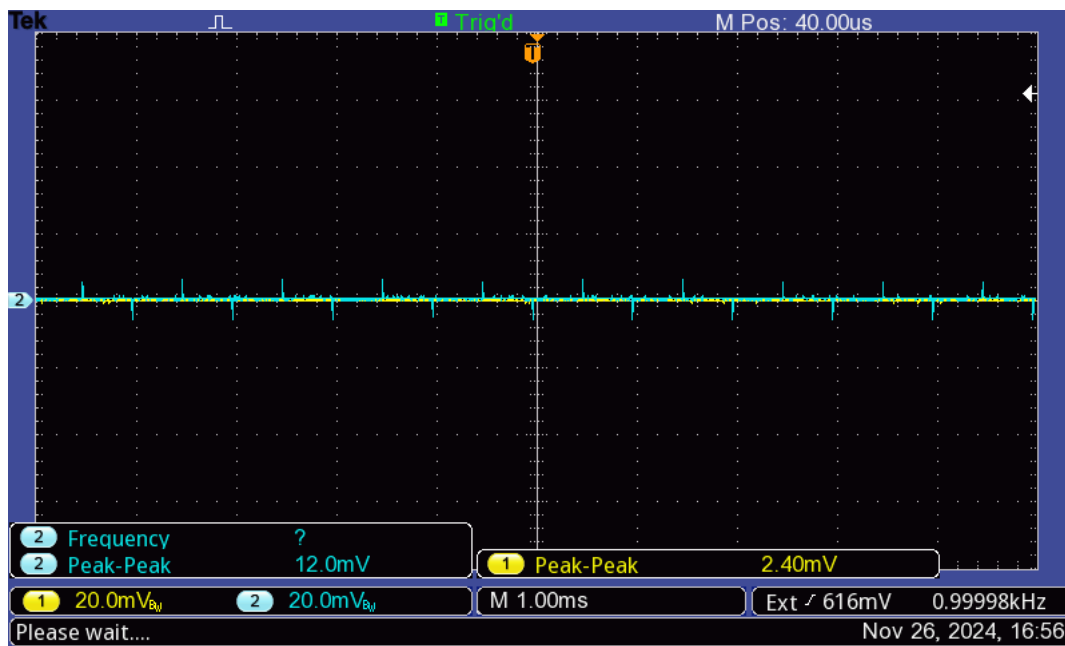

The output voltage in common mode is too small to be precisely measured by the oscilloscope, for the calculation I'll use the simulated value instead ( $21.93\mu\text{V}$  peak to peak).

Since the input is 100mV peak to peak

$$V_{vdm} = 20 \log \frac{3180}{100} = 30.05 \text{ dB}$$

$$V_{vcm} = 20 \log \frac{0.0219}{100} = -73.2 \text{ dB}$$

$$\text{CMRR} = 20 \log \frac{V_{vdm}}{V_{vcm}} = \frac{3180}{\frac{0.0219}{100}} = 83.2 \text{ dB}$$


## 3. Performance comparison

While using a fixed emitter resistor the differential voltage gain is almost the same as when using a current source (30.4dB vs 30.5dB), the common mode rejection ratio is around 224 times bigger when using a fixed current source (36.1dB vs 83.2dB).

### 3 Lab 3 Prelab


#### 3.1 Biasing of Bipolar Junction Transistor

##### 1. Calculations

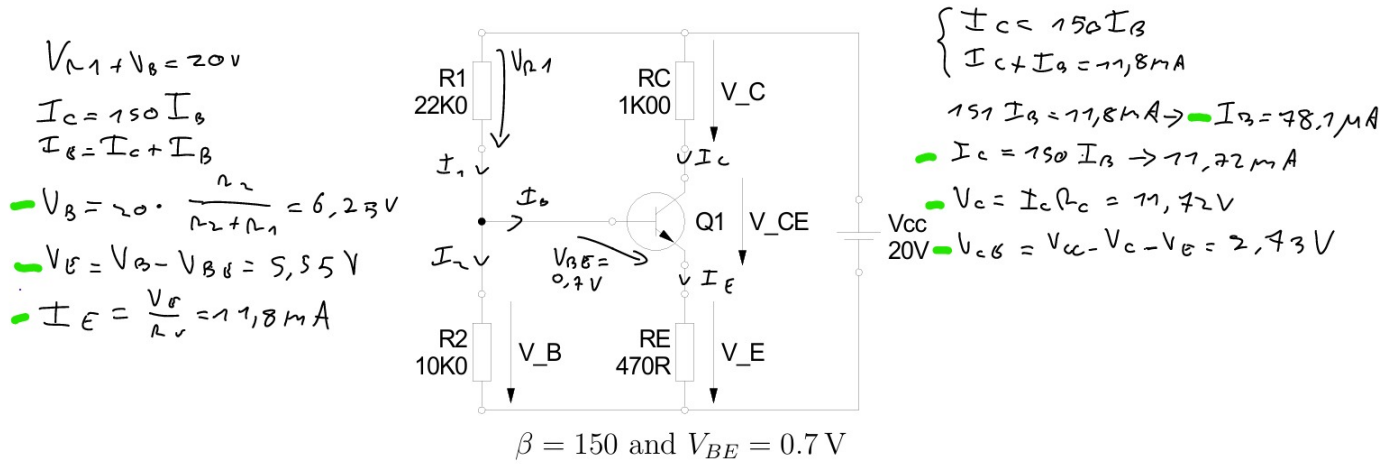


1. (a) Calculate  $V_B$ ,  $V_E$ ,  $V_{CE}$ , and  $V_C$ .
- (b) Calculate  $I_B$ ,  $I_E$ , and  $I_C$ .

##### LTSpice simulation

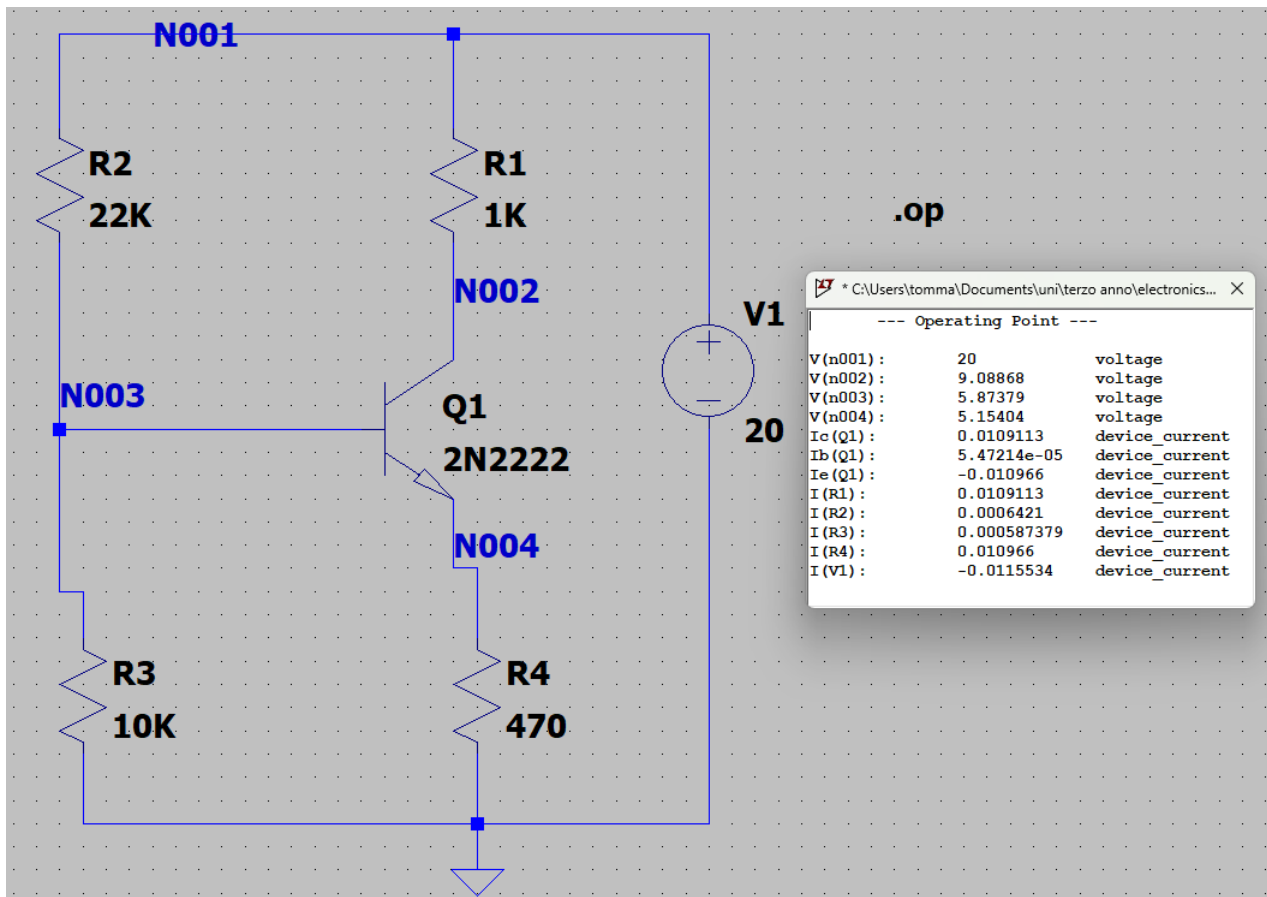


## 3.2 Constant Current Source
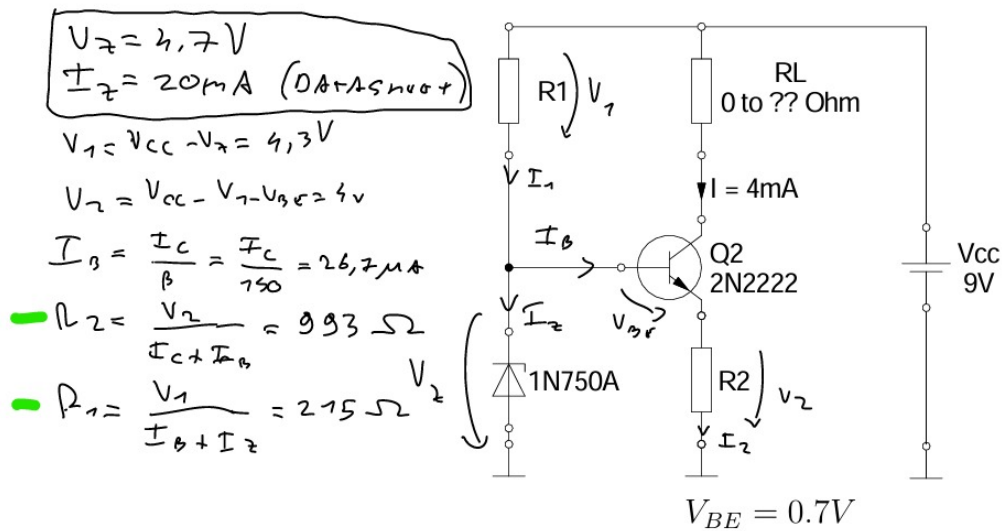
### 1. Calculations and simulation on LTSpice




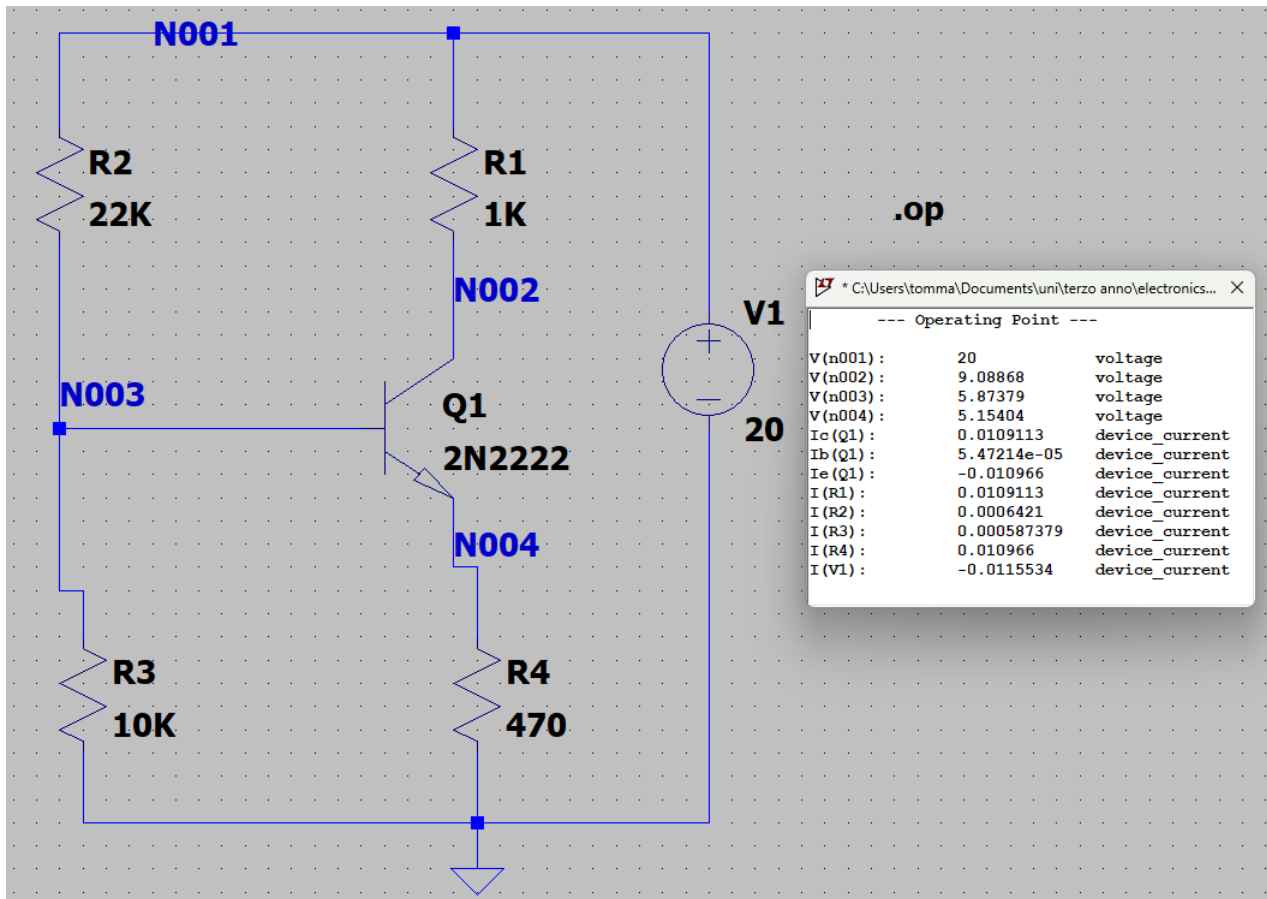2.  $R_1 = 215\Omega$ ,  $R_2 = 993\Omega$




3. To have a constant current  $V_{CE}$  has to be higher than  $0.3V$  (from 2N2222 datasheet) to stay in active mode. So the condition for  $R_L$  is  $V_{RL} < V_{CC} - 0.3V - V_2 = V_{RL} < 4.7V$  so  $R_L$  must be lower than  $\frac{4.7}{0.004} = 1175\Omega$ .

#### 4. Max $R_L$ in LTSpice

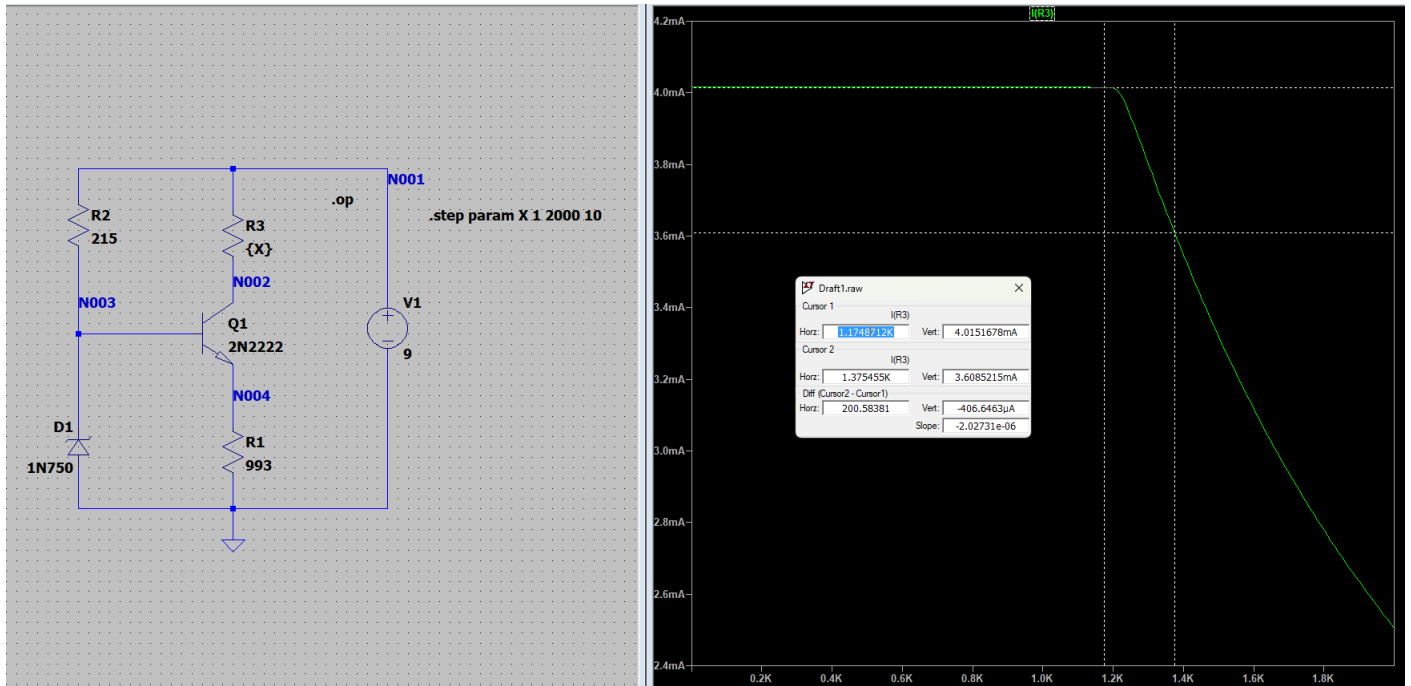

At  $1275\Omega$  the current is 4mA, at  $1375\Omega$  the current is 10% less (3.6mA).

### 3.3 Amplifier circuit

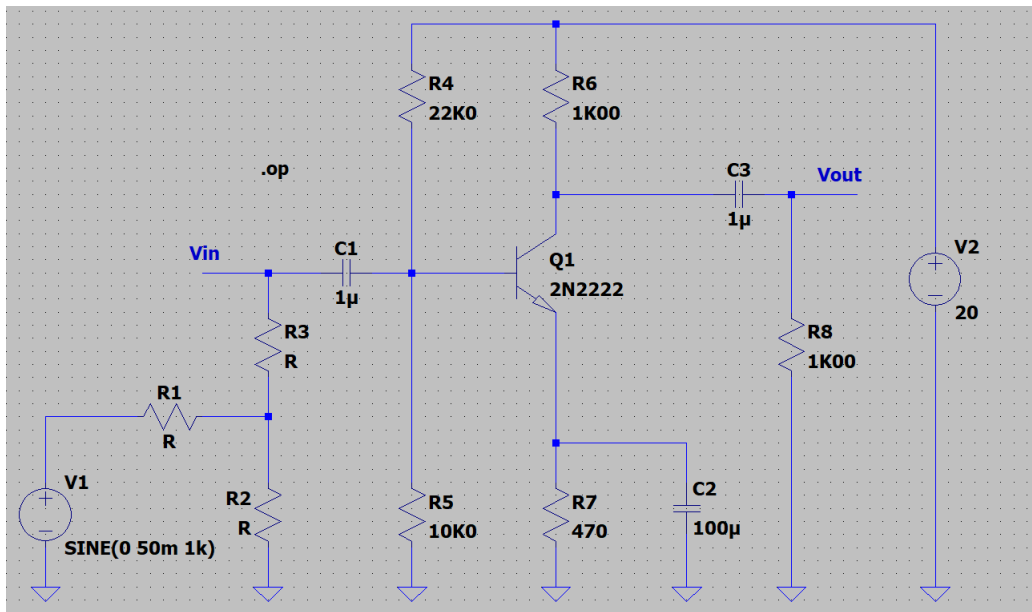


1.

#### 2. DC operation point values


$$I_C = 0.011 \text{ A}, I_B = 54.7 \text{ uA}$$

$$V_B = 5.87\text{V}, V_E = 5.15 \text{ V}, V_C = 9.09\text{V}, V_{BE} = 0.12, V_{CE} = 3.94\text{V}$$

### 3. Transient analysis at 50mV

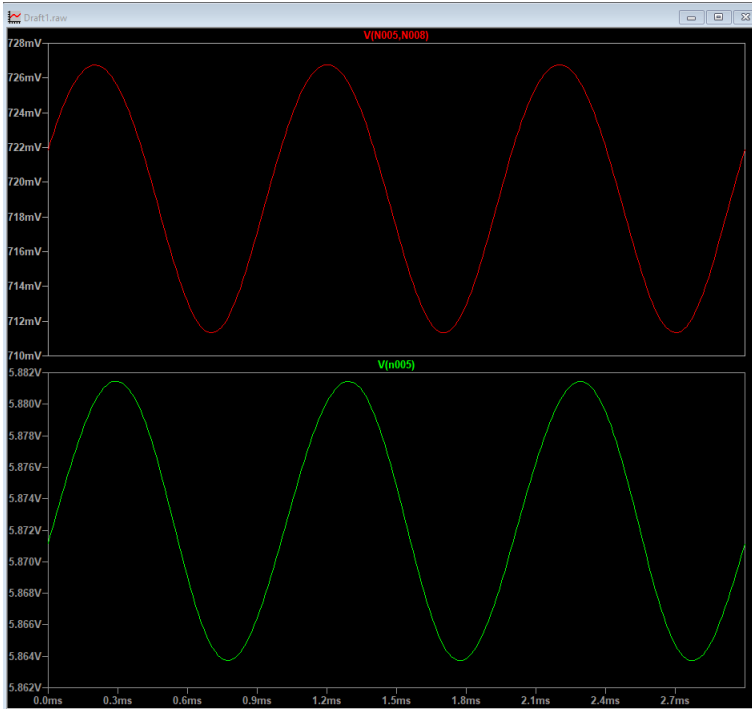

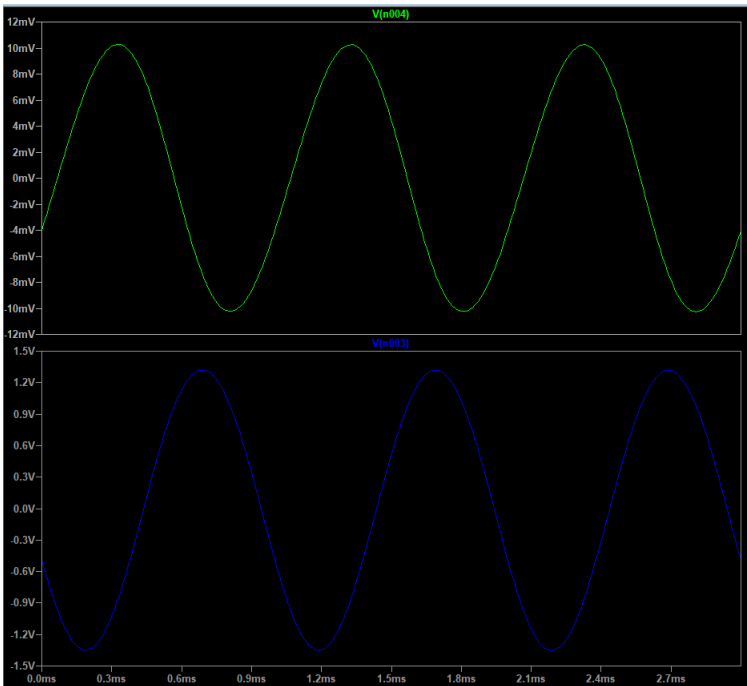
Green line:  $V_B$ : 17.7mV peak to peak, red line:  $V_{BE}$ : 15.4mV peak to peak.



Green line:  $V_i$ : 20.5mV peak to peak, blue line:  $V_o$ : 2.67V.



Gain:  $\frac{V_o}{V_i} = 130$ .

#### 4. Harmonic distortion analysis

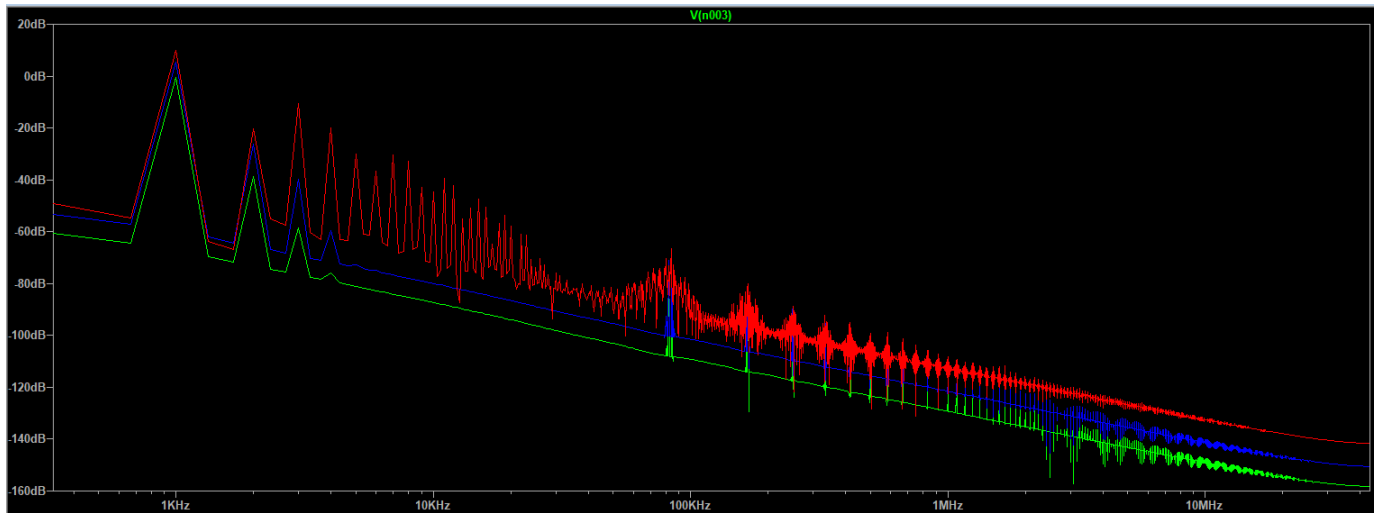

According to the FFT the harmonic distortion is similar between 50mV and 100mV as input amplitude and is much worse when using 200mV.

## 5. AC analysis

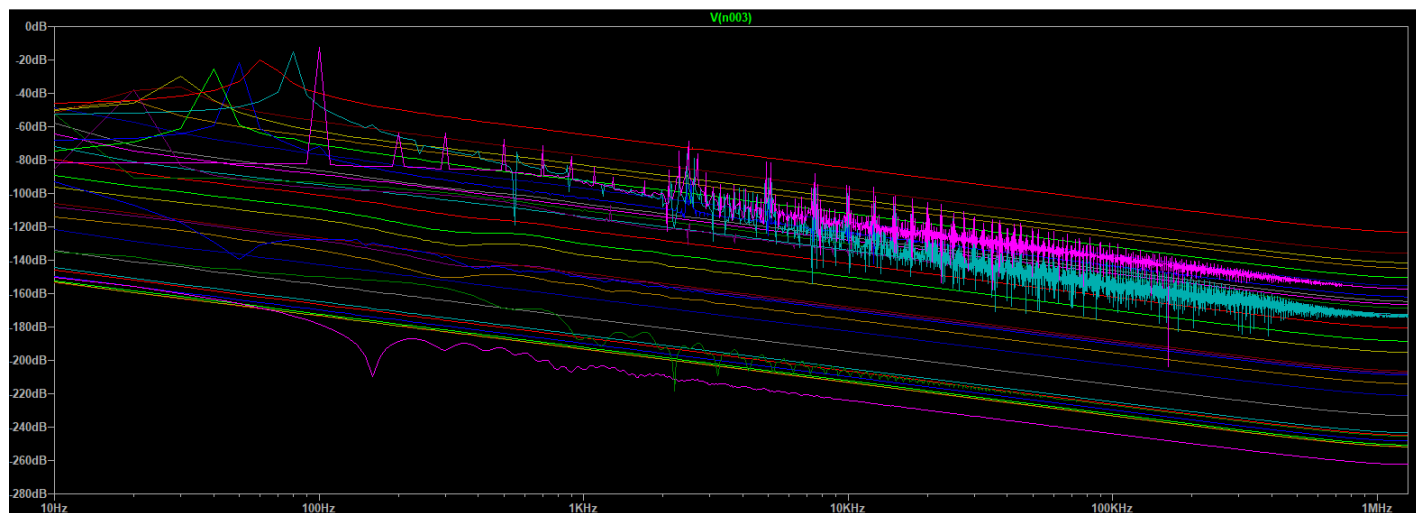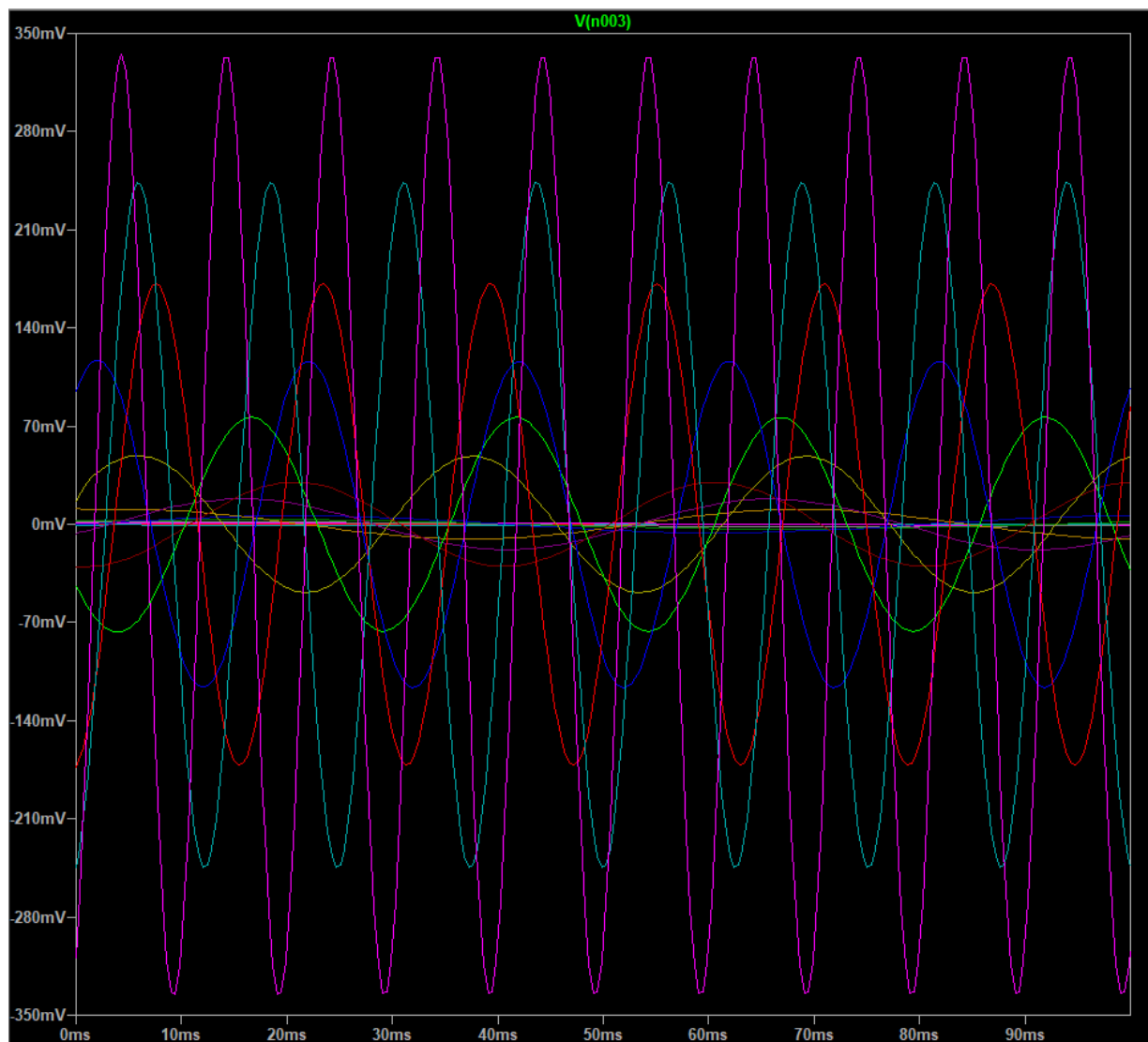

## 6. Bandwidth measurement

Lower -3dB frequency: 326.2 Hz  
Upper -3dB frequency: 479.5 kHz  
Bandwidth: 479.3 kHz