

Properties of the Differential Amplifier

Tommaso Bertelli

CO-526-B - Electronics Lab


Instructor Uwe Pagel

1/12/2024

1 Introduction - Prelab


1.1 Simulation of a Differential Amplifier

1.

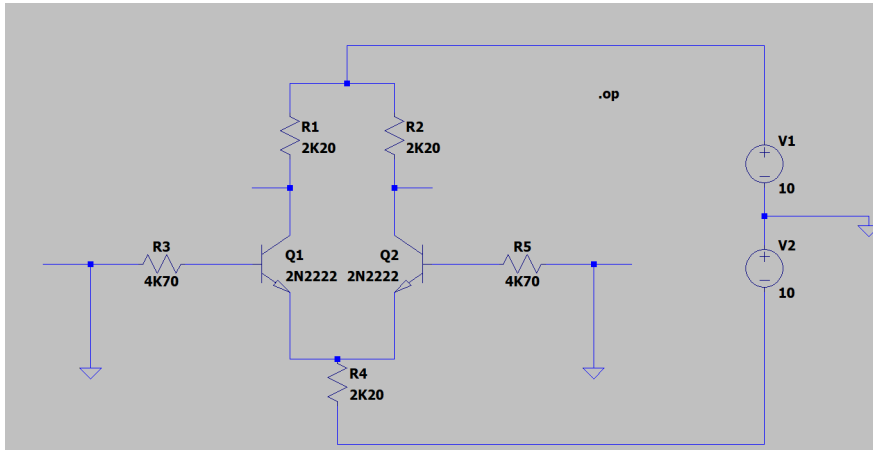



Measured voltages and currents:

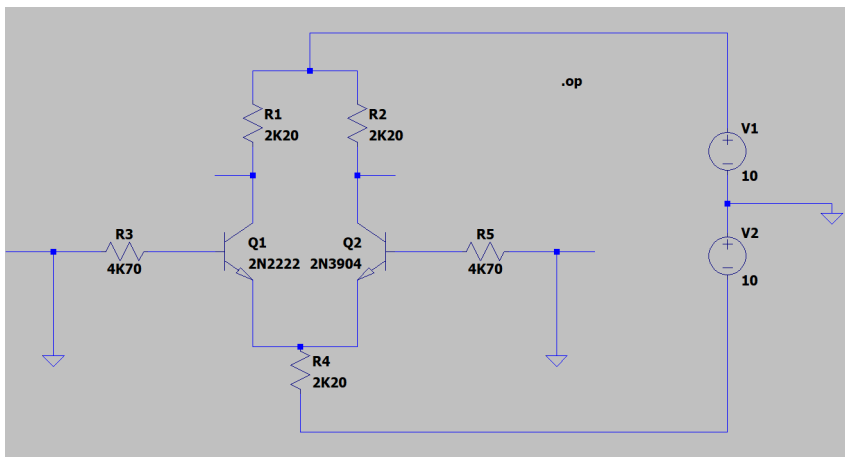$V_{BE} = -47.09 - (-720.71) = 767.8\text{mV}$, $V_C = 5.382\text{V}$, $I_C = 2.099\text{mA}$, $I_E = 2.109\text{mA}$, $I_{RE} = 4.219\text{mA}$.




By changing one transistor the V_{BE} , V_C , I_C , I_E values are not symmetric anymore (ex.: $V_C(Q1) = 5.911\text{V}$, $V_C(Q2) = 4.837\text{V}$), therefore the circuit cannot work properly.

2. Single ended input analysis

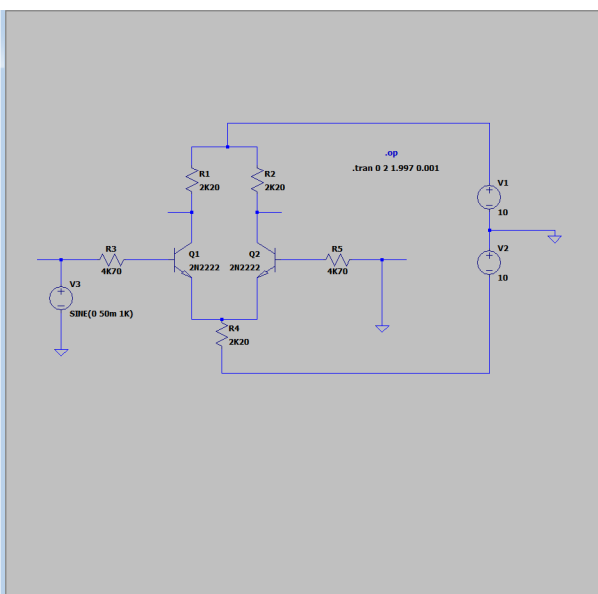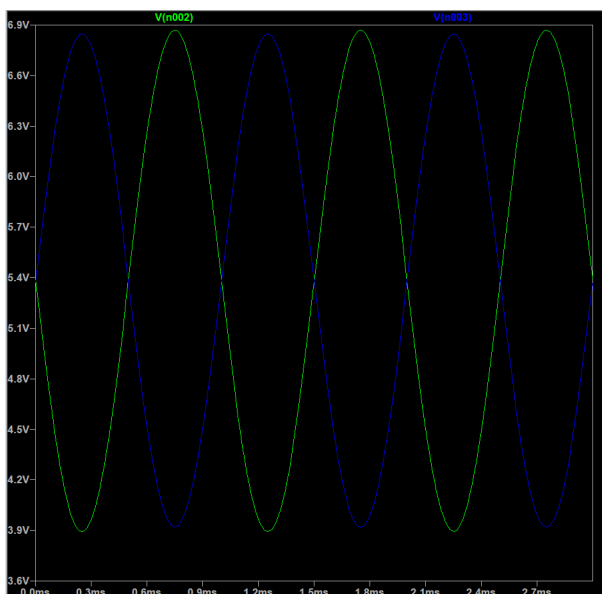

Green line: $V_C(Q1)$, blue line: $V_C(Q2)$. (peak to peak: 2.923V)

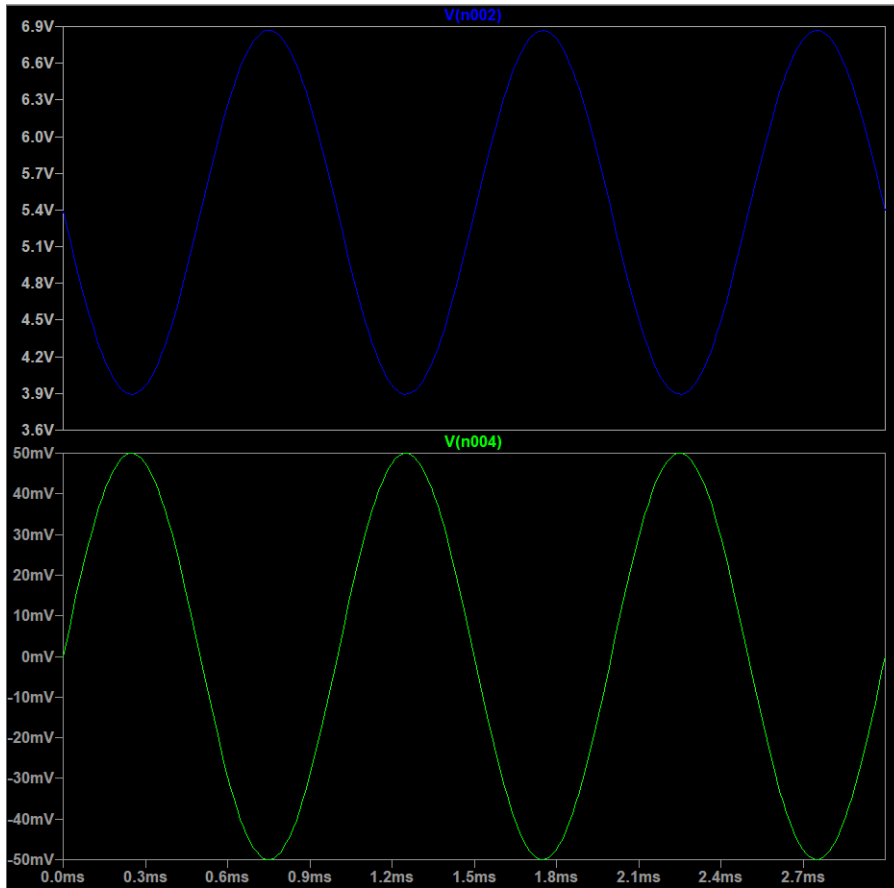To calculate $A_{V_{diff}}$ I need V_{od} and V_{id} .




Top pane: V_{o1} , bottom pane: V_{i1}

$V_{id} = V_{i1} - V_{i2} = 100\text{mV}$ peak to peak


$V_{od} = V_{o1} = 3\text{V}$ peak to peak

$A_{V_{diff}} = 20\log(\frac{V_{od}}{V_{id}}) = 29.5 \text{ dB}$.

3. Common mode input analysis

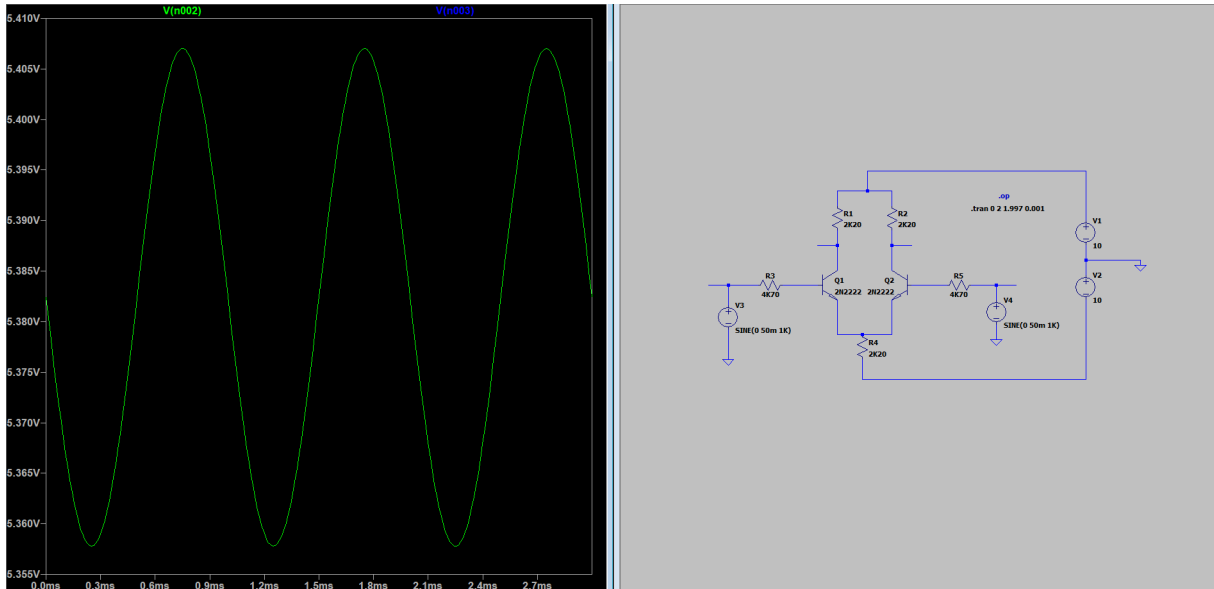

 $V_C(Q1)$ and $V_C(Q2)$ are overlapping. (peak to peak: 49.17mV).
To calculate $A_{V_{cm}}$ I need V_{oc} and V_{ic} .



Top pane: V_{o1} , bottom pane: V_{i1}

$$V_{ic} = (V_{i1} + V_{i2})/2 = 100\text{mV peak to peak}$$

$$V_{oc} = V_{o1} = 49.18\text{mV peak to peak}$$


$$A_{V_{cm}} = 20\log\left(\frac{V_{oc}}{V_{ic}}\right) = -6.16 \text{ dB.}$$

4. Common mode rejection

$$CMRR = 20\log\left(\frac{A_{V_{diff}}}{A_{V_{cm}}}\right) = 35.7\text{dB.}$$

current source: 4.219 from top to bottom

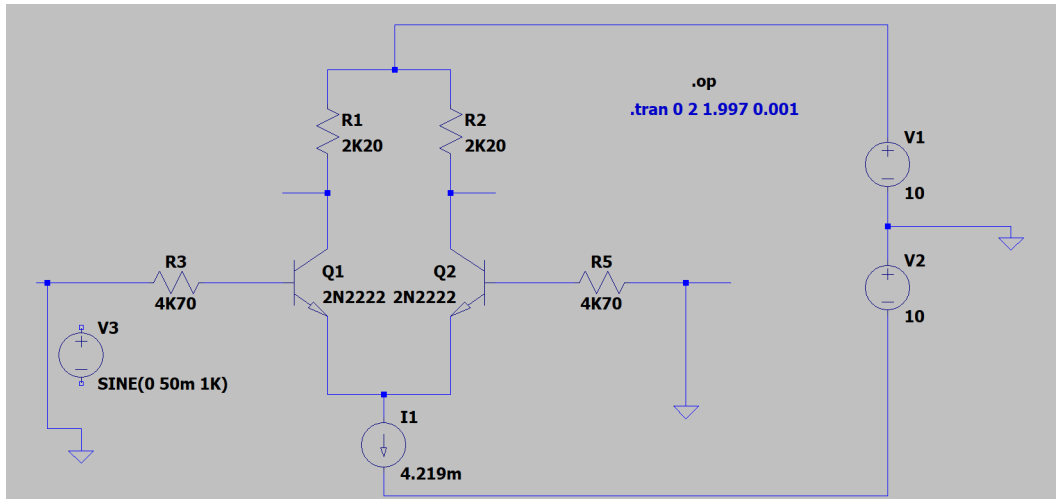
5. Replacing R4 by equivalent current source



6. Analyses using the current source

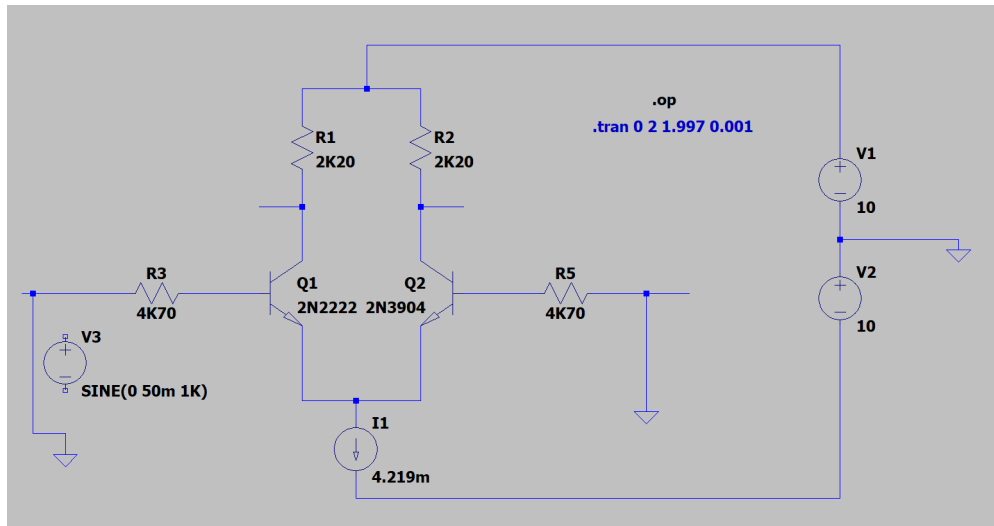
(a) DC operation point analysis

$V_{BE} = -47.11 - (-720.74) = 767.85\text{mV}$, $V_C = 5.381\text{V}$, $I_C = 2.099\text{mA}$, $I_E = 2.109\text{mA}$, $I_{RE} = 4.219\text{mA}$. (current source)




By changing one transistor the V_{BE} , V_C , I_C , I_E values are not symmetric anymore (ex.: $V_C(Q1) = 5.913\text{V}$, $V_C(Q2) = 4.841\text{V}$), therefore the circuit cannot work properly.

(b) Single ended input analysis

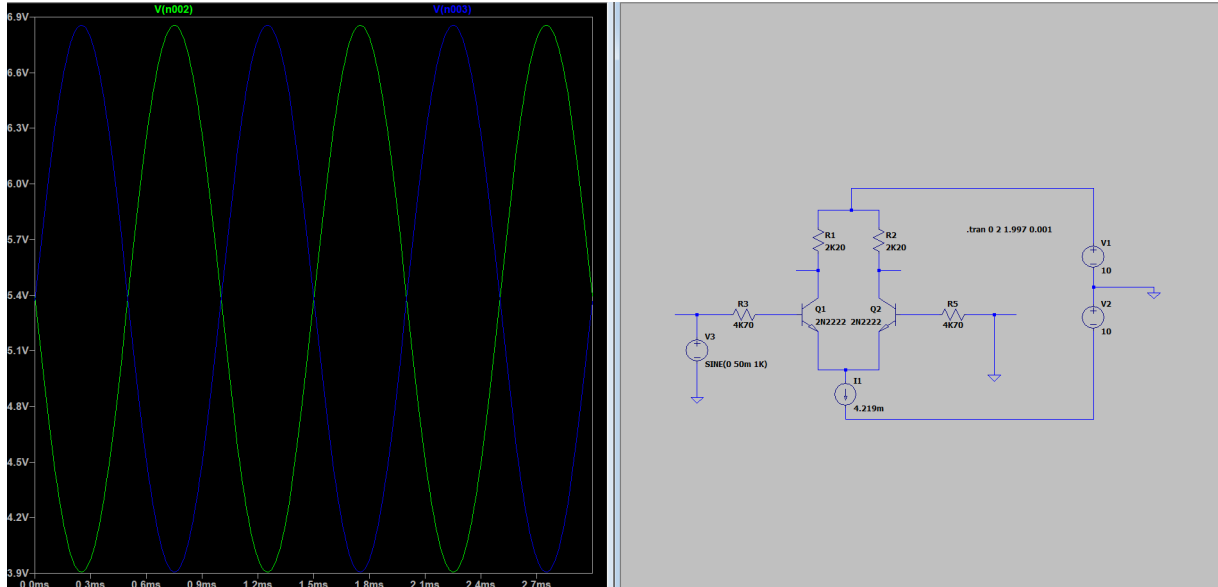

Green line: $V_C(Q1)$, blue line: $V_C(Q2)$. (peak to peak: 2.95V)

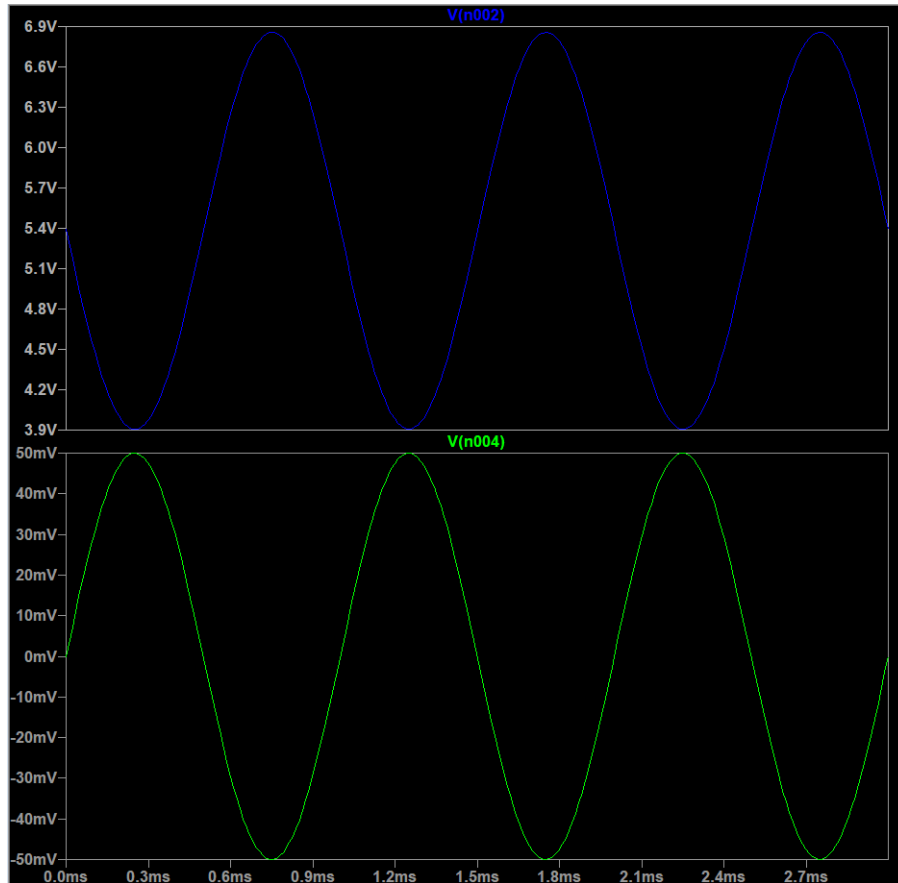To calculate $A_{V_{diff}}$ I need V_{od} and V_{id} .




Top pane: V_{o1} , bottom pane: V_{i1}

$V_{id} = V_{i1} - V_{i2} = 100\text{mV}$ peak to peak

$V_{od} = V_{o1} = 2.95\text{V}$ peak to peak


$A_{V_{diff}} = 20\log\left(\frac{V_{od}}{V_{id}}\right) = 29.4 \text{ dB}$.

(c) Common mode input analysis

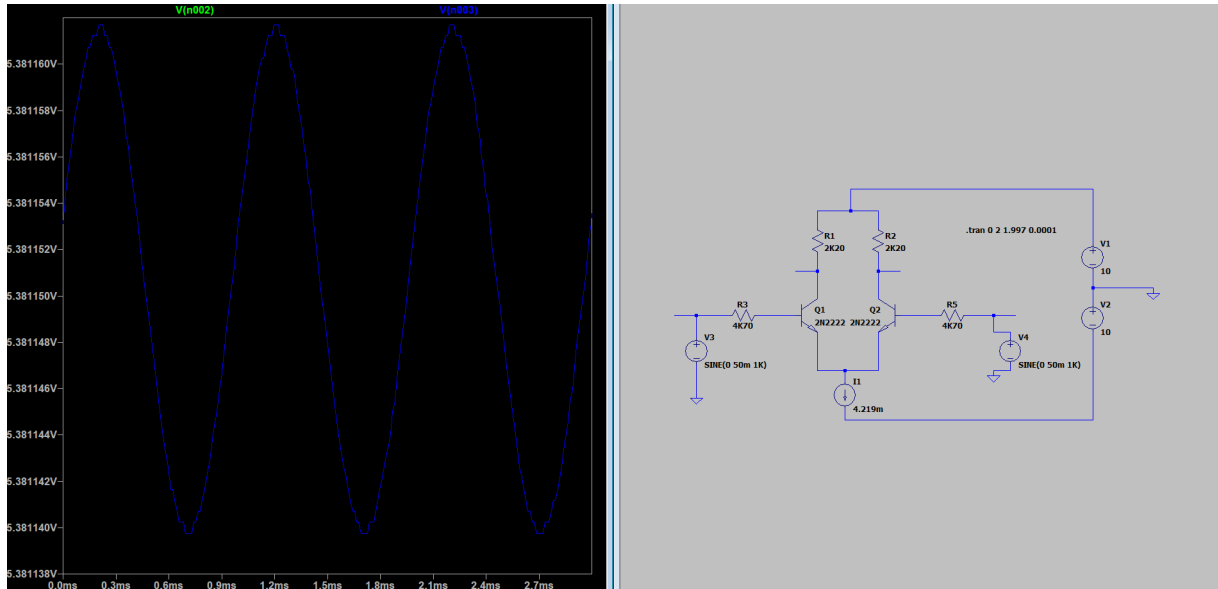

$V_C(Q1)$ and $V_C(Q2)$ are overlapping. (peak to peak: $21.93\mu\text{V}$).

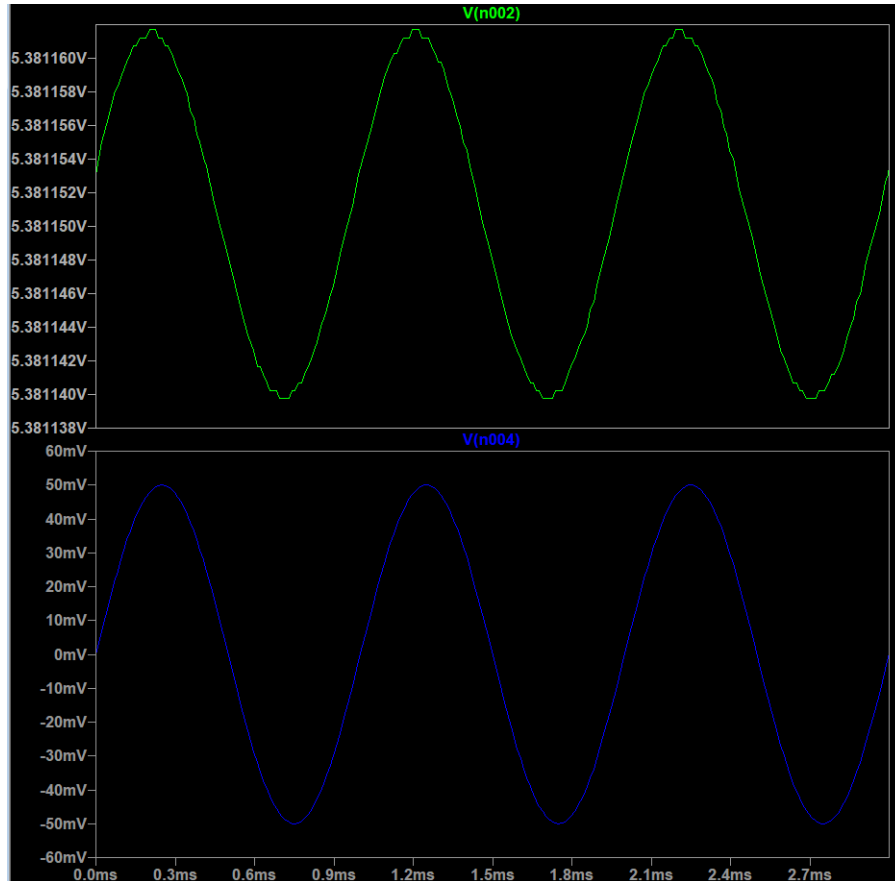To calculate $A_{V_{cm}}$ I need V_{oc} and V_{ic} .



Top pane: V_{o1} , bottom pane: V_{i1}

$$V_{ic} = (V_{i1} + V_{i2})/2 = 100\text{mV peak to peak}$$

$$V_{oc} = V_{o1} = 21.93\mu\text{V peak to peak}$$

$$A_{V_{cm}} = 20\log\left(\frac{V_{oc}}{V_{ic}}\right) = -73.28 \text{ dB.}$$

(d) Common mode rejection

$$CMRR = 20\log\left(\frac{A_{V_{diff}}}{A_{V_{cm}}}\right) = 102.6\text{dB.}$$


2 Experimental Set-up and Results

2.1 Differential amplifier using a fixed emitter resistor


1. Experimental DC bias values: $V_B(T_1, T_2) = 5.680\text{V}$, $V_B(T_1, T_2) = 45.6\text{mV}$, $V_{BE}(T_1, T_2) = 634.1\text{mV}$, $I_{RE} = 1.93\text{mA}$.
Some reasons for the differences between the simulated values and the measured ones could be the following:
 - (a) Transistor calibration: the bjts in the simulation are identical while, on the experiment, the two bjts used are sold in multiple numbers and not calibrated to be pairs as identical as possible.
 - (b) Temperature difference: the most temperature sensitive voltages (ex: V_{BE}) could be different since the ambient temperature in the lab is not monitored while the assumed temperature in the simulation is always 25°C .
 - (c) Parasitic Effects: using a breadboard, there could be parasitic capacities and resistances due to the prototypical wiring and the fact that used resistors are not precise and could have induced some imbalances in the supposed symmetric circuit.

2. CMRR calculation

Output voltage in single ended mode:

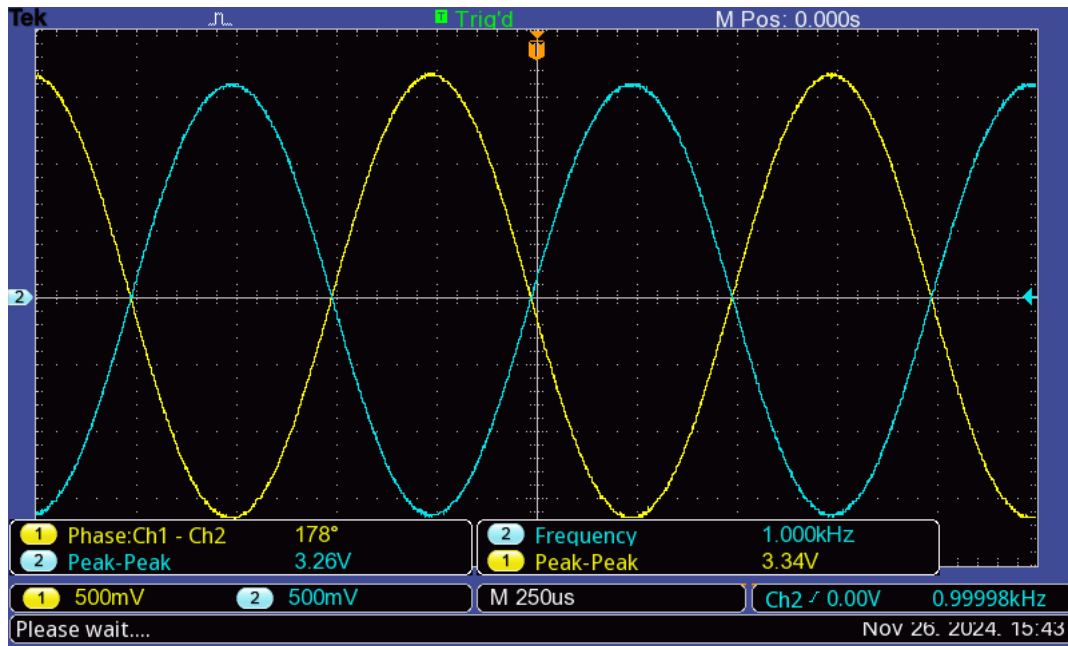

Output voltage in common mode:

 

Since the input is 100mV peak to peak

$$V_{vdm} = 20 \log \frac{3300}{100} = 30.4 \text{ dB}$$

$$V_{vcm} = 20 \log \frac{51.5}{100} = -5.76 \text{ dB}$$

$$\text{CMRR} = 20 \log \frac{V_{vdm}}{V_{vcm}} = \frac{3300}{\frac{51.5}{100}} = 36.1 \text{ dB}$$

2.2 Differential amplifier using a current source


1. Experimental DC bias values: $V_B(T_1, T_2) = 5.612\text{V}$, $V_B(T_1, T_2) = 0.040\text{V}$, $V_{BE}(T_1, T_2) = 0.63\text{V}$, $I_C(T_1, T_2) = 2.08\text{mA}$, $I_{RE} = 3.92\text{mA}$.

Some reasons for the differences between the simulated values and the measured ones could be the following:


- (a) Transistor calibration: the bjts in the simulation are identical while, on the experiment, the two bjts used are sold in multiple numbers and not calibrated to be pairs as identical as possible.
- (b) Temperature difference: the most temperature sensitive voltages (ex: V_{BE}) could be different since the ambient temperature in the lab is not monitored while the assumed temperature in the simulation is always 25°C .
- (c) Parasitic Effects: using a breadboard, there could be parasitic capacities and resistances due to the prototypical wiring and the fact that used resistors are not precise (ex: R1 in the current source circuit was supposed to be 530Ω but we used a 530Ω one) and could have induced some imbalances in the supposed symmetric circuit.

2. CMRR calculation

Output voltage in single ended mode:

 

Output voltage in common mode:

 

The output voltage in common mode is too small to be precisely measured by the oscilloscope, for the calculation I'll use the simulated value instead ($21.93\mu\text{V}$ peak to peak).

Since the input is 100mV peak to peak

$$V_{vdm} = 20 \log \frac{3180}{100} = 30.05\text{dB}$$

$$V_{vcm} = 20 \log \frac{0.0219}{100} = -73.2\text{dB}$$

$$\text{CMRR} = 20 \log \frac{V_{vdm}}{V_{vcm}} = \frac{3180}{\frac{0.0219}{100}} = 83.2\text{dB}$$

3. Performance comparison

While using a fixed emitter resistor the differential voltage gain is almost the same as when using a current source (30.4dB vs 30.5dB), the common mode rejection ratio is around 224 times bigger when using a fixed current source (36.1dB vs 83.2dB).

3 Lab 3 Prelab

3.1 Biasing of Bipolar Junction Transistor

1. Calculations

$$V_{R1} + V_B = 20V$$


$$I_C = 150 I_B$$

$$I_E = I_C + I_B$$

$$V_B = 20 \cdot \frac{R_2}{R_2 + R_1} = 6,23V$$

$$V_E = V_B - V_{BE} = 5,55V$$

$$I_E = \frac{V_E}{R_E} = 11,8\mu A$$

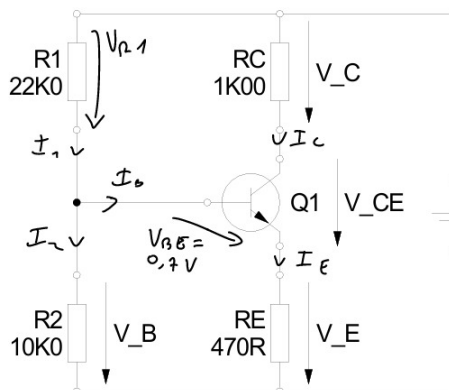

$$\begin{cases} I_C < 150 I_B \\ I_C + I_B = 11,8\mu A \end{cases}$$

$$151 I_B = 11,8\mu A \Rightarrow I_B = 78,1\mu A$$

$$I_C = 150 I_B \rightarrow 11,72\mu A$$


$$V_C = I_C R_C = 11,72V$$

$$V_{CE} = V_{CC} - V_C - V_E = 2,73V$$

$$\beta = 150 \text{ and } V_{BE} = 0.7V$$


1. (a) Calculate V_B , V_E , V_{CE} , and V_C .
- (b) Calculate I_B , I_E , and I_C .

LTSpice simulation

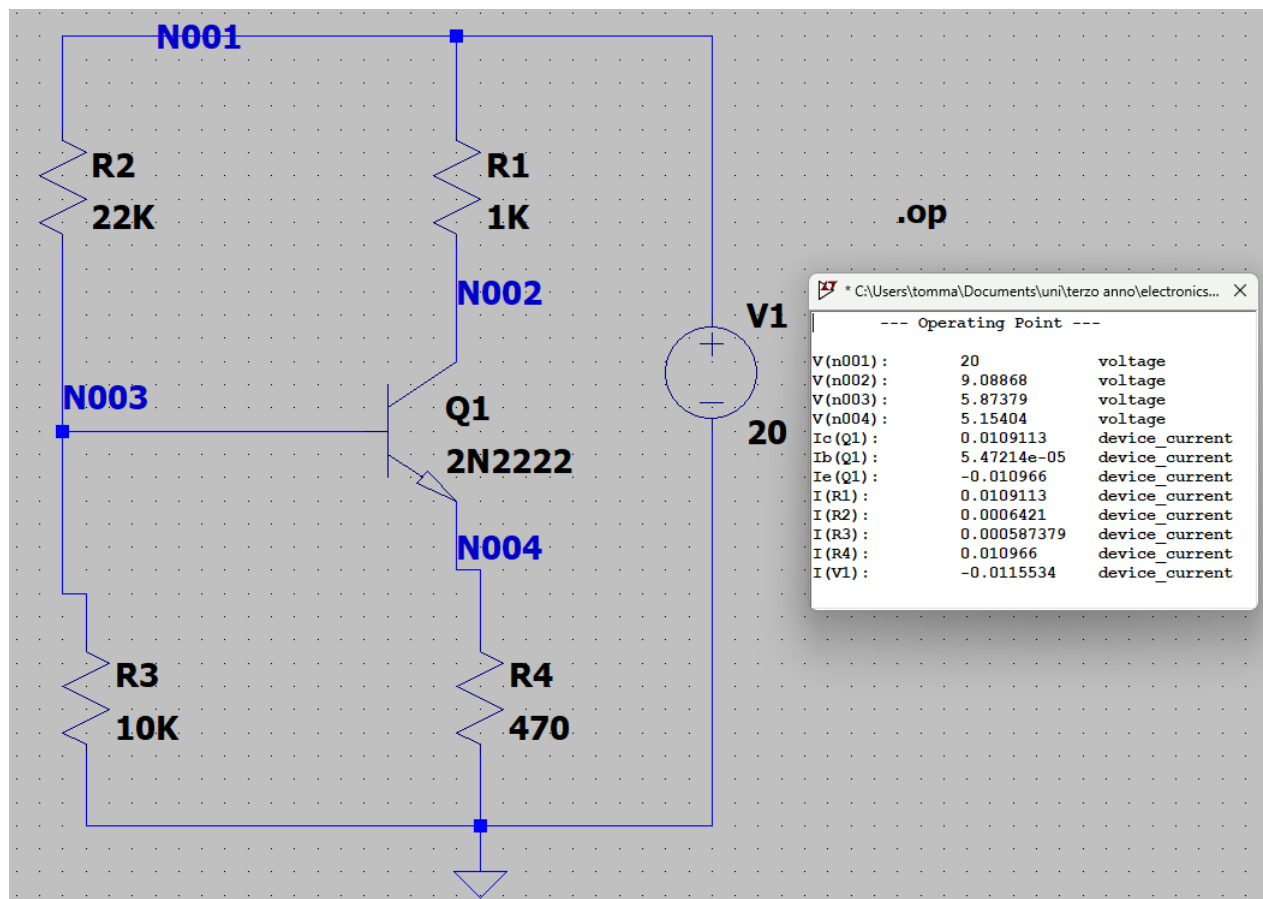


3.2 Constant Current Source

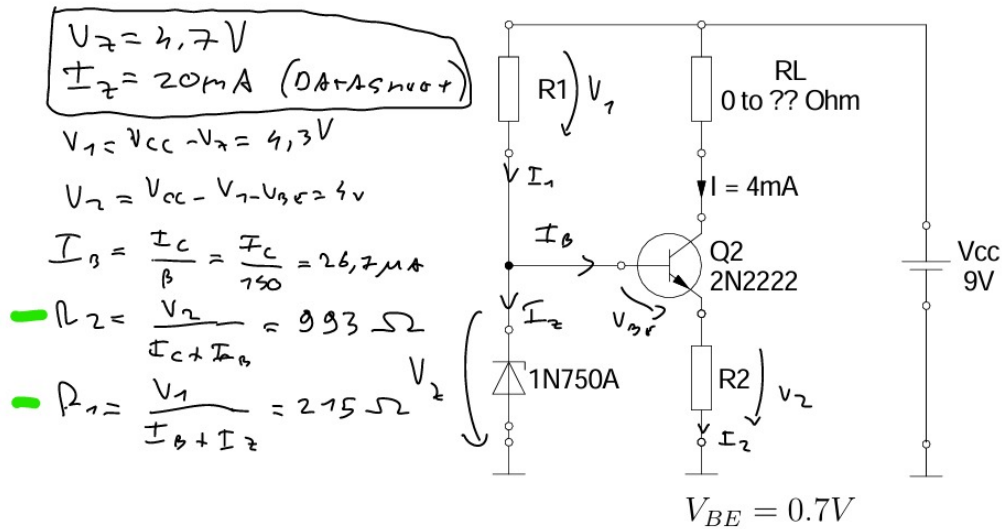1. Calculations and simulation on LTSpice




2. $R_1 = 215\Omega$, $R_2 = 993\Omega$

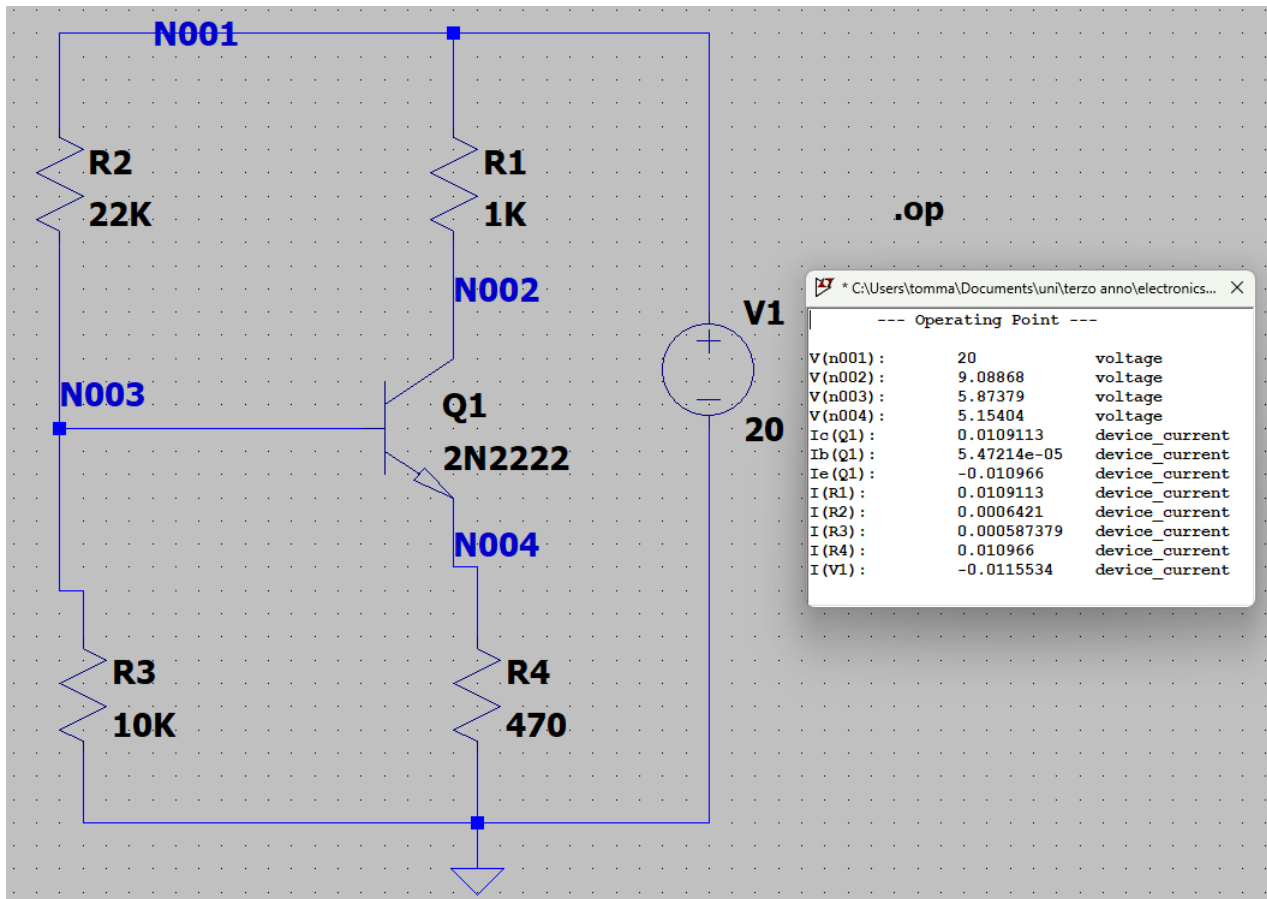


3. To have a constant current V_{CE} has to be higher than $0.3V$ (from 2N2222 datasheet) to stay in active mode. So the condition for R_L is $V_{RL} < V_{CC} - 0.3V - V_2 = V_{RL} < 4.7V$ so R_L must be lower than $\frac{4.7}{0.004} = 1175\Omega$.

4. Max R_L in LTSpice

 

At 1275Ω the current is 4mA, at 1375Ω the current is 10% less (3.6mA).

3.3 Amplifier circuit

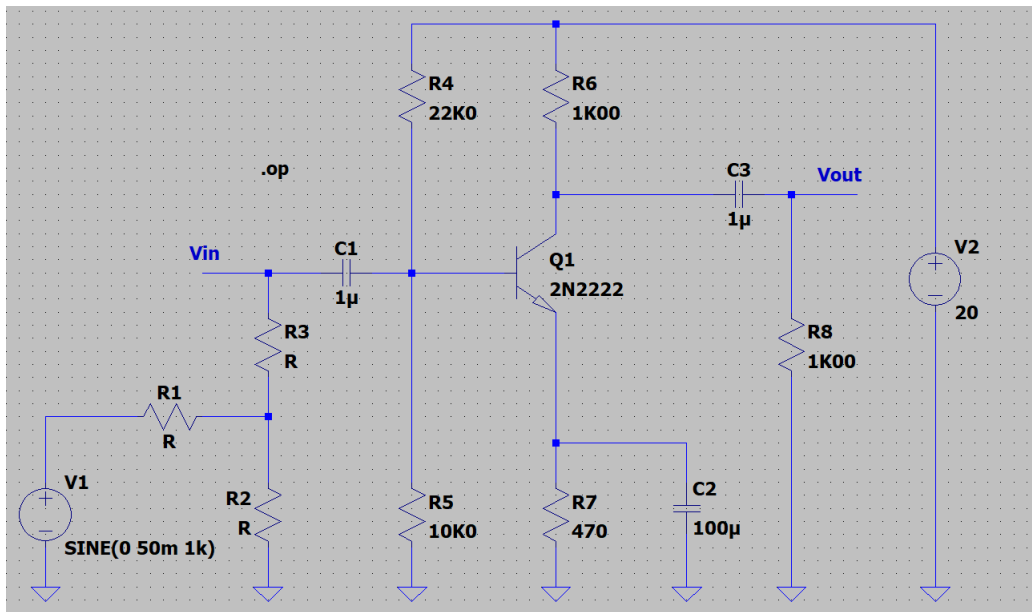


1.

2. DC operation point values


$$I_C = 0.011 \text{ A}, I_B = 54.7 \text{ uA}$$

$$V_B = 5.87\text{V}, V_E = 5.15 \text{ V}, V_C = 9.09\text{V}, V_{BE} = 0.12, V_{CE} = 3.94\text{V}$$

3. Transient analysis at 50mV

 

 
Green line: V_B : 17.7mV peak to peak, red line: V_{BE} : 15.4mV peak to peak.



Green line: V_i : 20.5mV peak to peak, blue line: V_o : 2.67V.



Gain: $\frac{V_o}{V_i} = 130$.

4. Harmonic distortion analysis

 

According to the FFT the harmonic distortion is similar between 50mV and 100mV as input amplitude and is much worse when using 200mV.

5. AC analysis

  

6. Bandwidth measurement

Lower -3dB frequency: 326.2 Hz
Upper -3dB frequency: 479.5 kHz
Bandwidth: 479.3 kHz